


Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science

6.002 – Circuits & Electronics
Spring 2007
Homework #9
Handout - S07-45


Issued 4/12/2007 – Due 4/20/2007

Helpful Reading for this Homework: Chapter 12.

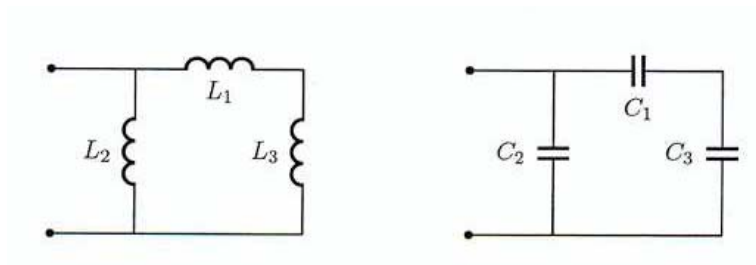
Exercise 9.1. Find the inductance of the all-inductor network, and the capacitance of the all-capacitor network, shown below.



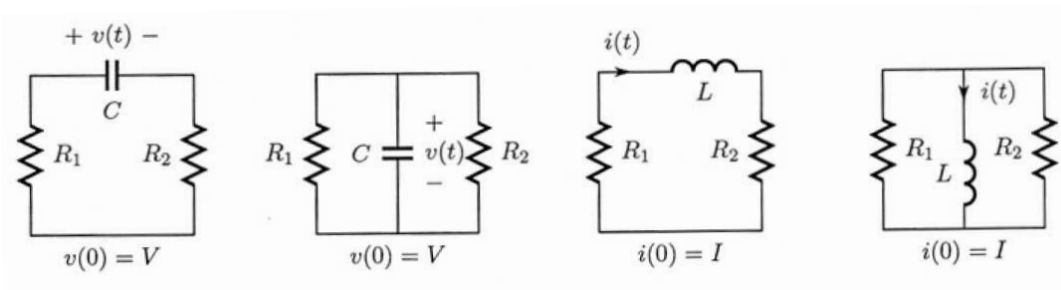Exercise 9.2. Each network shown below has a non-zero initial state at $t = 0$ s, as indicated. Find the network states for $t \geq 0$ s. Hint: what equivalent resistance is in parallel with each capacitor or inductor, and what decay time results from this combination?




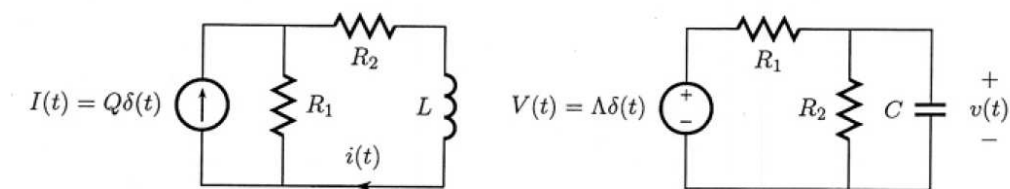Problem 9.1. At $t = 0^-$ s, the networks shown below have zero initial state; the inductor current $i(t)$ and the capacitor voltage $v(t)$ are both zero at $t = 0^-$ s. At $t = 0$ s, the current source produces an impulse of area Q , and the voltage source produces an impulse of area Λ .



- A Derive the differential equation that relates $i(t)$ to $I(t)$ and $v(t)$ to $V(t)$. Hint: consider using Thevenin and/or Norton equivalents to simplify the work.
- B Find the inductor current $i(t)$ and the capacitor voltage $v(t)$ at both $t = 0^+$ s and $t = \infty$. Feel free to determine the states through either physical or mathematical reasoning. However, explain your reasoning in any case.
- C Next, find the time constant by which each state goes from its initial value at $t = 0^+$ s to its final value at $t = \infty$.
- D Using the previous results, and without necessarily solving the differential equations directly, construct $i(t)$ and $v(t)$ for $t \geq 0$ s. Alternatively, find $i(t)$ and $v(t)$ by any means you choose, but be sure to explain your reasoning.
- E Verify that the solutions to part D are correct by substituting them into the differential equations found in part A.

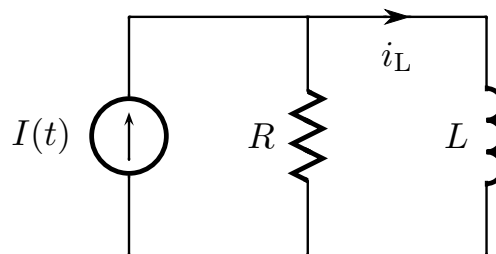
Problem 9.2. This problem examines the relation between transient responses of linear systems.



- A Find the inductor current $i_L(t)$ for $t \geq 0$ s in response to the current step $I(t) = I_{Step}(t) = I_0u(t)$. Assume that $i(0) = 0$.
- B Find the inductor current $i_L(t)$ for $t \geq 0$ s in response to the current step $I(t) = I_{Ramp}(t) = I_0\alpha t u(t)$. Again, assume that $i(0) = 0$.
- C The step input can be constructed from the ramp input according to $I_{Step}(t) = \frac{1}{\alpha} \frac{d}{dt} I_{Ramp}(t)$. Show that their respective responses are related in a similar manner. (Note: you could have used this relation to solve part B given your answer to part A.)
- D Would the result from part C hold if $i(0) \neq 0$? Why or why not?

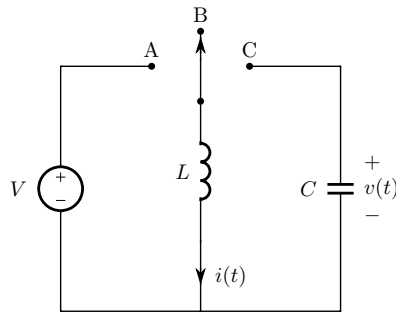Problem 9.3. The network shown at the top of next page includes a switch with three positions: A, B and C. Prior to $t = 0$ s, the switch is in Position B, and the inductor current $i(t)$ and the capacitor voltage $v(t)$ are both zero. The voltage source V is constant.

- A At $t = 0$ the switch moves to Position A, and it remains there until $t = T_1$. Find $i(t)$ and $v(t)$ for $0 \leq t \leq T_1$.
- B At $t = T_1$ the switch moves to Position C without interrupting the current $i(t)$, and it remains there until $i(t)$ goes to zero, at which time the switch moves back to Position B. Define the time at which $i(t)$ goes to zero as $t = T_2$. Determine T_2 , and find both $i(t)$ and $v(t)$ for $T_1 \leq t \leq T_2$.



- C** The switch remains in Position B until $t = T_3$. Find both $i(t)$ and $v(t)$ for $T_2 \leq t \leq T_3$
- D** At $t = T_3$ the switch moves again to Position A , and it remains there until $t = T_4$. Find $i(t)$ and $v(t)$ for $T_3 \leq t \leq T_4$.
- E** Finally, at $t = T_4$ the switch moves to Position C , and it remains there until $i(t)$ first goes to zero, at which time the switch moves back to Position B . Define the time at which $i(t)$ again goes to zero as T_5 . Determine T_5 , and find both $i(t)$ and $v(t)$ for $T_4 \leq t \leq T_5$.
- F** Sketch and clearly label $i(t)$ and $v(t)$ for $0 \leq t \leq T_5$

Problem 9.4. This problem is continuation of Problem 9.3. It explores the use of energy conservation to analyze the operation of the network described therein.

- A** Determine the energy stored in the inductor at $t = T_1$.
- B** The energy stored in the inductor at $t = T_1$ is fully transferred to the capacitor at $t = T_2$. Use this fact to determine $v(T_2)$. This answer should match your answer in part B of Problem 9.3 when the latter is evaluated at $t = T_2$.
- C** Determine the energy stored in the inductor at $t = T_4$.
- D** Use energy conservation to determine the energy stored in the capacitor at $t = T_5$, and then determine $v(T_5)$. This answer should match your answer to part E of Problem 9.3 when the latter is evaluated at $t = T_5$.
- E** Now let the switch move repetitively through the cycle of Positions B to A to C to B . Assume that in each cycle the switch remains in Position A for the duration T . Further, assume that switch always moves from Position C to Position B when $i(t)$ reaches zero. Assuming that v and i are initial zero, determine v at the end of the n^{th} switching cycle in terms of n, C, L, T and V .