

6.002

**CIRCUITS AND
ELECTRONICS**


Operational Amplifier Circuits

Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

6.002 Fall 2000 Lecture 20

Review

■ Operational amplifier abstraction

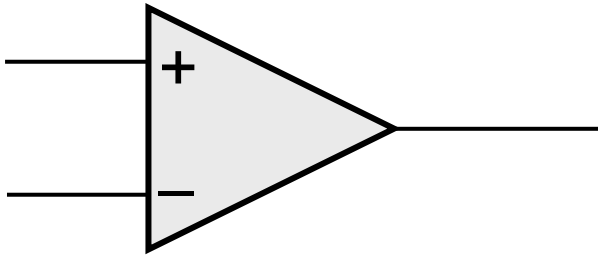

- ◆ ∞ input resistance
- ◆ 0 output resistance
- ◆ Gain " A " very large

■ Building block for analog systems

■ We will see these examples:

Digital-to-analog converters

Filters

Clock generators


Amplifiers

Adders

Integrators & Differentiators

Reading: Chapter 15.5 & 15.6 of A & L.

Consider this circuit:

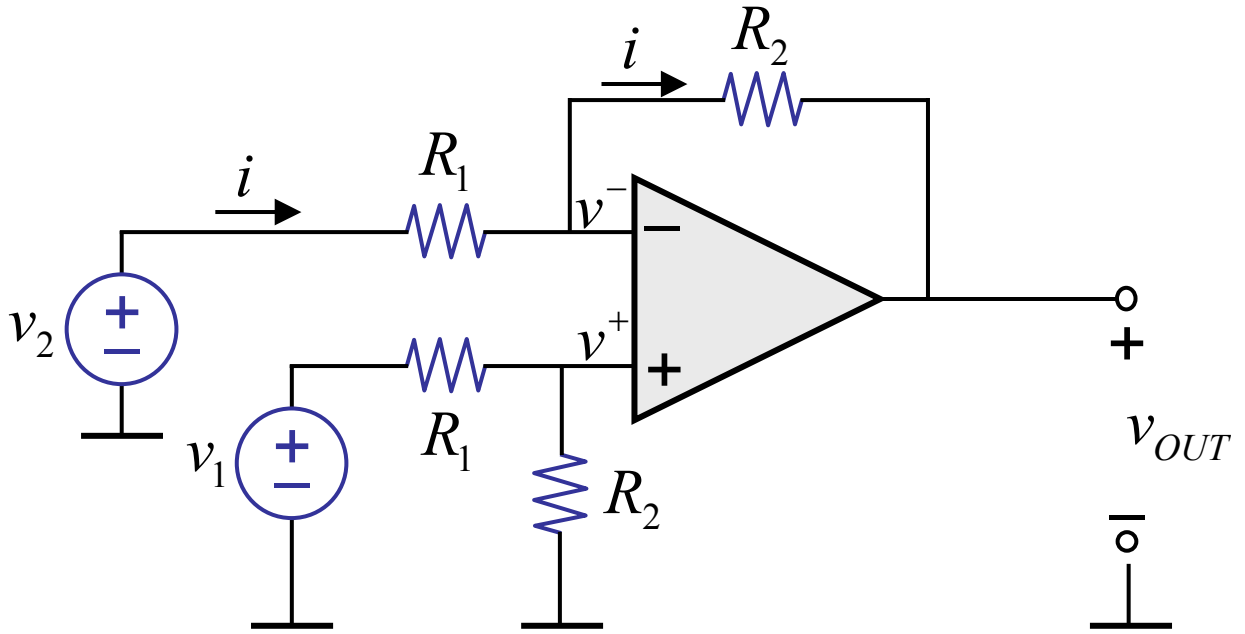

$$v^+ = v_1 \frac{R_2}{R_1 + R_2}$$

$$\approx v^-$$

$$i = \frac{v_2 - v^-}{R_1}$$

$$v_{OUT} = v^- - iR_2$$

$$= v^- - \frac{v_2 - v^-}{R_1} \cdot R_2$$


$$= v^- \left[1 + \frac{R_2}{R_1} \right] - v_2 \frac{R_2}{R_1}$$

$$= v_1 \frac{R_2}{\cancel{R_1 + R_2}} \cdot \frac{\cancel{R_1 + R_2}}{R_1} - v_2 \frac{R_2}{R_1}$$


$$= \frac{R_2}{R_1} (v_1 - v_2)$$

subtracts!

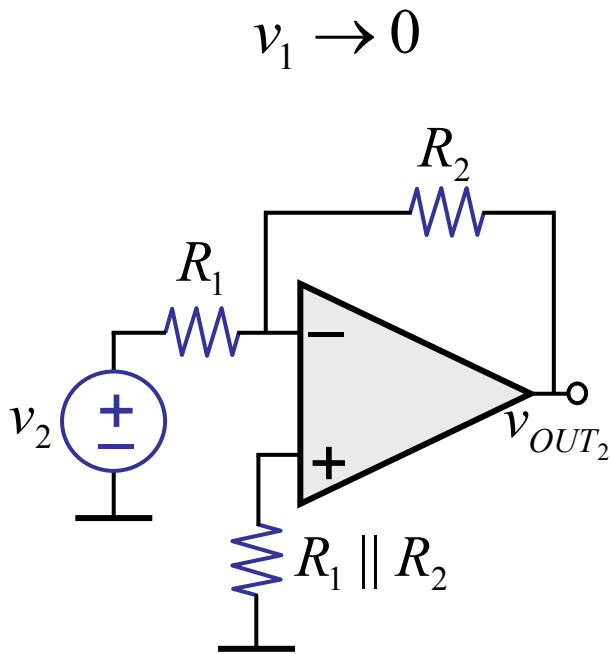Another way of solving — use superposition



$$v_{OUT_2} = -\frac{R_2}{R_1} v_2$$

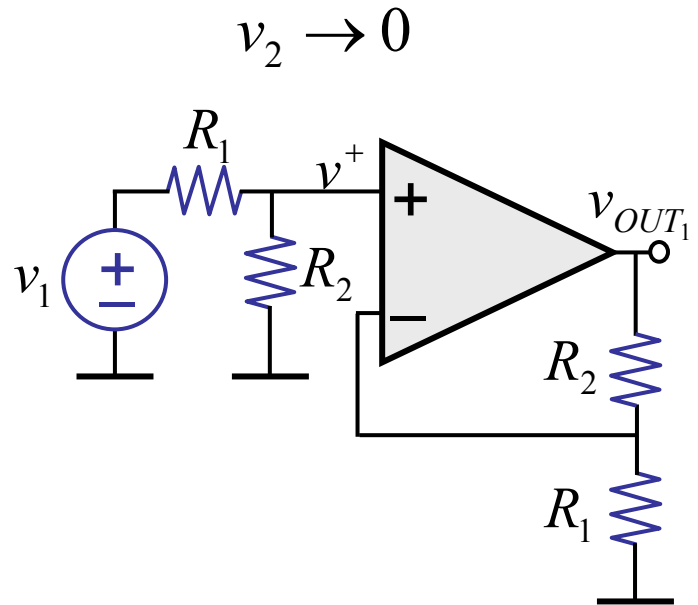


$$\begin{aligned} v_{OUT_1} &= v^+ \cdot \frac{R_1 + R_2}{R_1} \\ &= \frac{v_1 \cdot R_2}{R_1 + R_2} \cdot \frac{R_1 + R_2}{R_1} \\ &= v_1 \frac{R_2}{R_1} \end{aligned}$$


$$\begin{aligned} v_{OUT} &= v_{OUT_1} + v_{OUT_2} \\ &= \frac{R_2}{R_1} (v_1 - v_2) \end{aligned}$$

Still subtracts!

Let's build an intergrator...

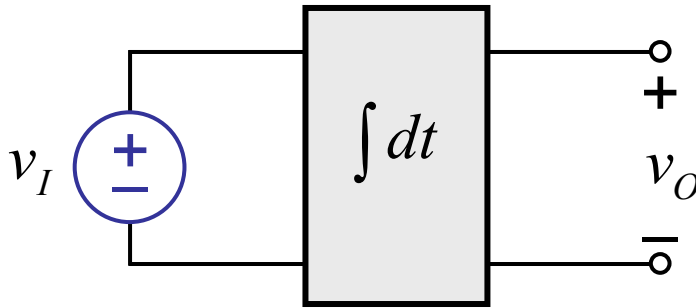

Let's start with the following insight:

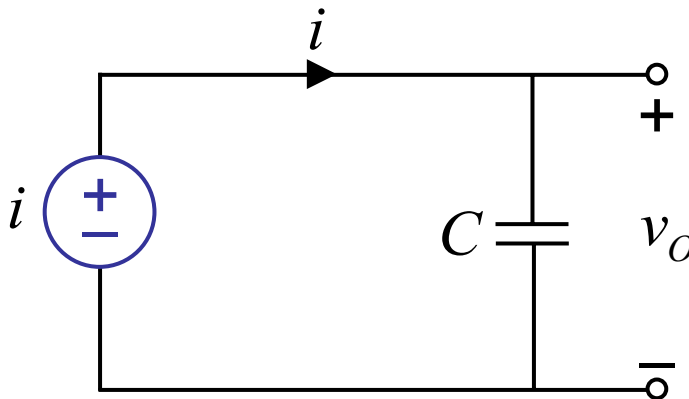


$$v_O = \frac{1}{C} \int_{-\infty}^t i dt$$

v_O is related to $\int i dt$

But we need to somehow convert voltage v_I to current.

First try... use resistor

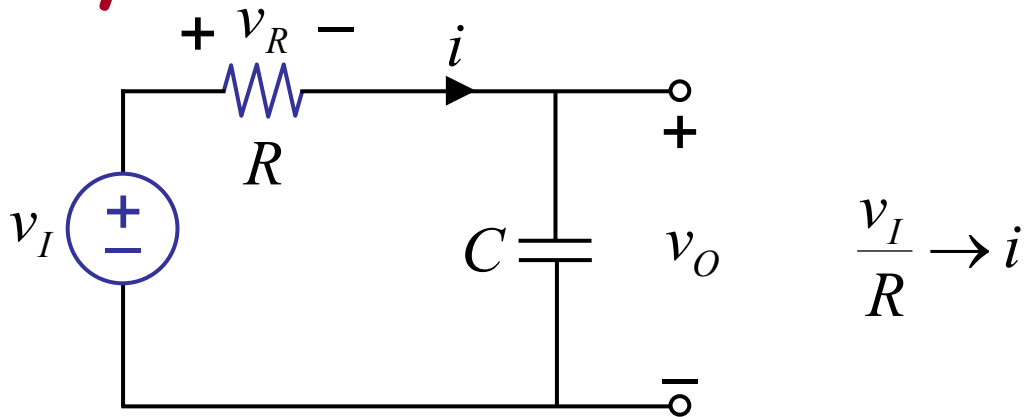

But, v_O must be very small compared to v_R , or else

$$i \neq \frac{v_I}{R}$$

When is v_O small compared to v_R ?

$$\underbrace{RC \frac{dv_O}{dt}}_{v_R} + v_O = v_I \quad \longrightarrow \quad \text{larger the } RC, \text{ smaller the } v_O$$

when $RC \frac{dv_O}{dt} \gg v_O$

$$RC \frac{dv_O}{dt} \approx v_I$$


or $v_O \approx \frac{1}{RC} \int_{-\infty}^t v_I dt$

for good
integrator
 $\omega RC \gg 1$





There's a better way...

Notice

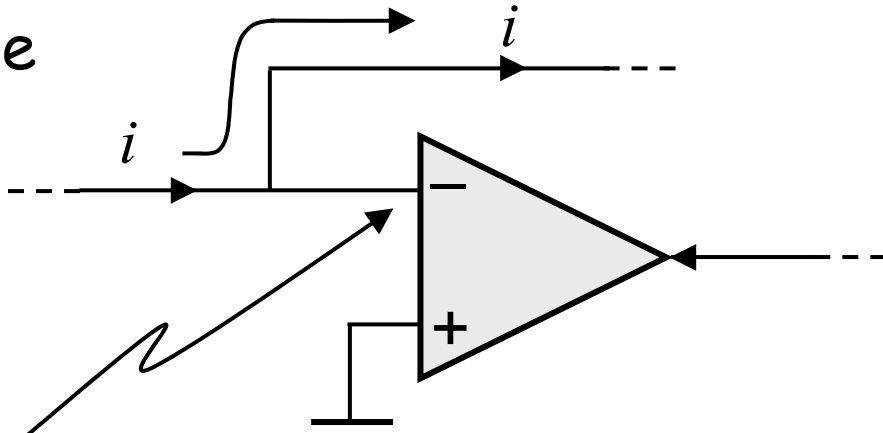

$v^- \approx 0V$ under negative feedback


so, $i = \frac{v_I}{R}$

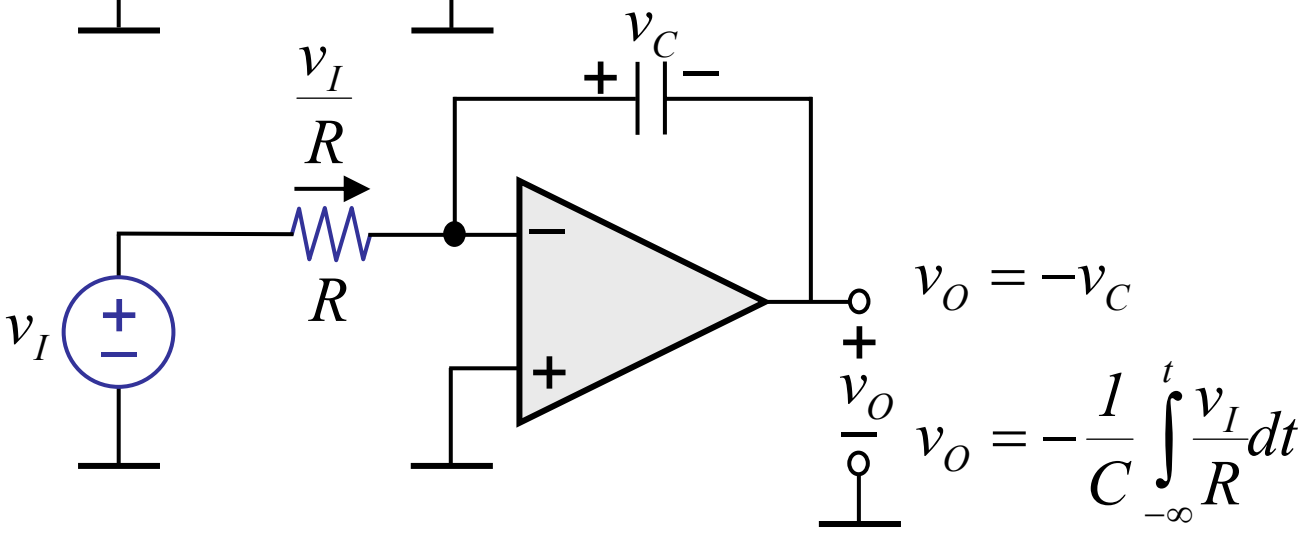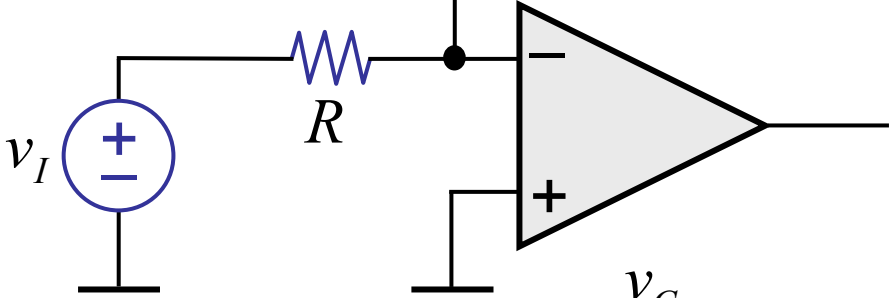


We have our integrator.

Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

Now, let's build a differentiator...

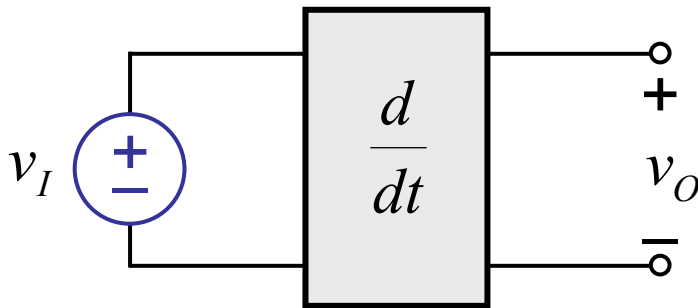

Let's start with the following insights:


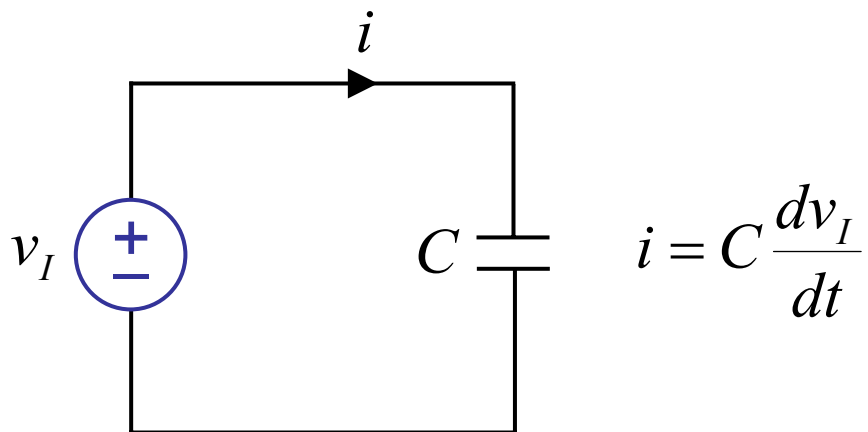


i is related to $\frac{dv_I}{dt}$


But we need to somehow convert current to voltage.

Recall

Differentiator...

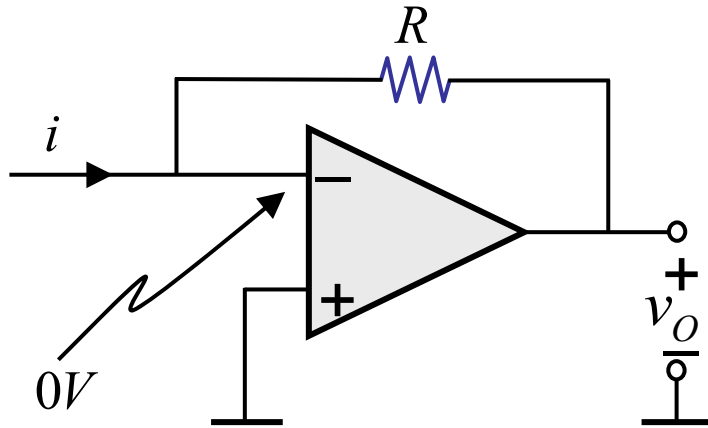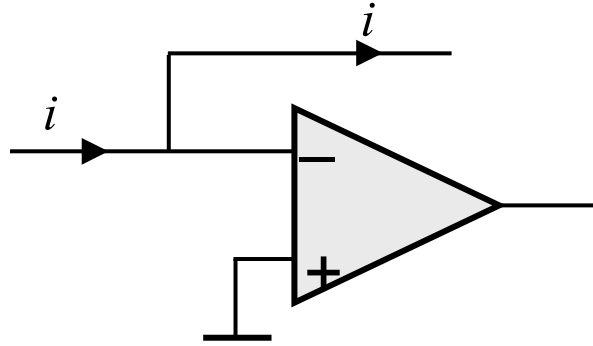

$v_O = -iR$
current
to
voltage

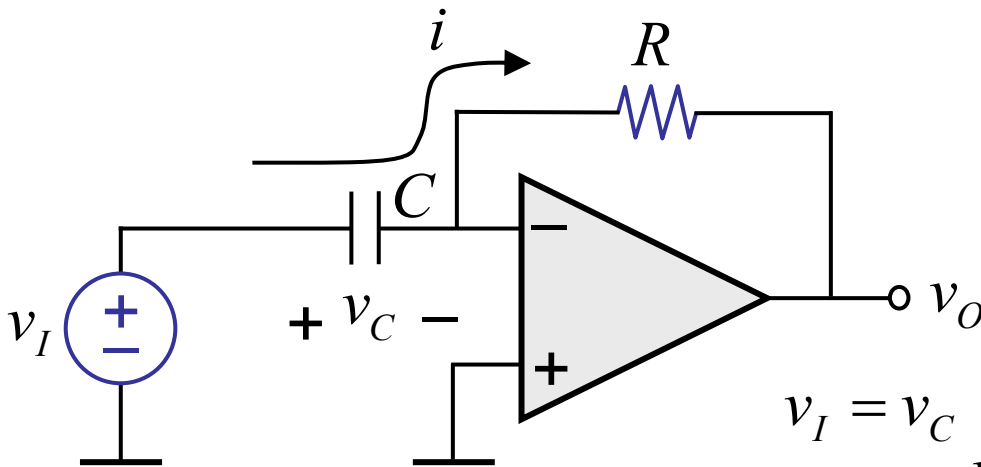

$$v_I = v_C$$

$$i = C \frac{dv_I}{dt}$$

$$v_O = -RC \frac{dv_I}{dt}$$

