

MIT OpenCourseWare
<http://ocw.mit.edu>

6.004 Computation Structures
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.

Building the Beta



Figure by MIT OpenCourseWare.

Lab #5 due Thursday

CPU Design Tradeoffs

Maximum Performance: measured by the numbers of instructions executed per second

Minimum Cost: measured by the size of the circuit.

Best Performance/Price: measured by the ratio of MIPS to size. In power-sensitive applications MIPS/Watt is important too.

Performance Measure

Millions of Instructions per Second

$$\text{MIPS} = \frac{\text{Clock Frequency (MHz)}}{\text{C.P.I.}}$$


Clocks per instruction

PUSHING PERFORMANCE ...


TODAY: 1 cycle/inst.

LATER: more MHz via pipelining

The Beta ISA

 

 Operate class: $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{Reg}[Rb]$



Operate class: $\text{Reg}[Rc] \leftarrow \text{Reg}[Ra] \text{ op } \text{SXT}(C)$

OpCodes, both formats:

ADD SUB MUL* DIV* *optional
CMFEQ CMPL CMPLT
AND OR XOR
SHL SHR SRA



LD: $\text{Reg}[Rc] \leftarrow \text{Mem}[\text{Reg}[Ra] + \text{SXT}(C)]$
ST: $\text{Mem}[\text{Reg}[Ra] + \text{SXT}(C)] \leftarrow \text{Reg}[Rc]$
JMP: $\text{Reg}[Rc] \leftarrow \text{PC} + 4; \text{PC} \leftarrow \text{Reg}[Ra]$
BEQ: $\text{Reg}[Rc] \leftarrow \text{PC} + 4; \text{if } \text{Reg}[Ra] = 0 \text{ then } \text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SXT}(C)$
BNE: $\text{Reg}[Rc] \leftarrow \text{PC} + 4; \text{if } \text{Reg}[Ra] \neq 0 \text{ then } \text{PC} \leftarrow \text{PC} + 4 + 4 * \text{SXT}(C)$
LDR: $\text{Reg}[Rc] \leftarrow \text{Mem}[\text{PC} + 4 + 4 * \text{SXT}(C)]$

Instruction classes distinguished by OPCODE:
OP
OPC
MEM
MEM
Transfer of Control


Approach: Incremental Featurism

Each instruction class can be implemented using a simple component repertoire. We'll try implementing data paths for each class individually, and merge them (using MUXes, etc).


Steps:

1. Operate instructions
2. Load & Store Instructions
3. Jump & Branch instructions
4. Exceptions
5. Merge data paths

Our Bag of Components:

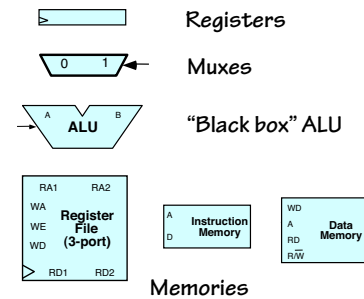


Multi-Port Register Files

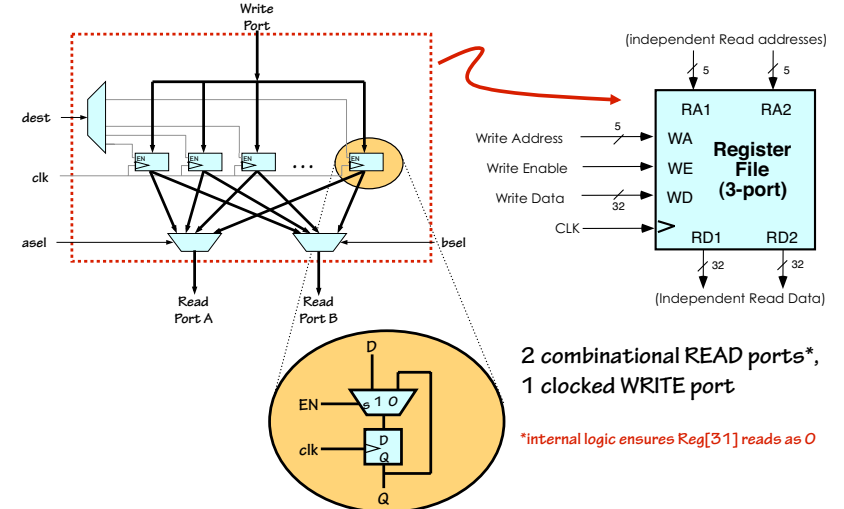

Register File Timing

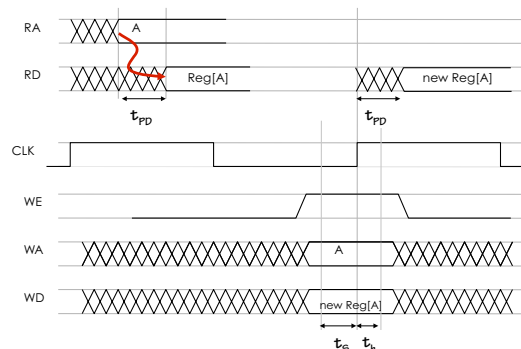2 combinational READ ports, 1 clocked WRITE port



What if (say) $WA=RA1$???

RD1 reads “old” value of Reg[RA1] until next clock edge!

Starting point: ALU Ops

32-bit (4-byte) ADD instruction:

`10000000010000010000110000000000`

OpCode Rc Ra Rb (unused)


Means, to BETA, $Reg[R4] \leftarrow Reg[R2] + Reg[R3]$

First, we'll need hardware to:

- Read next 32-bit instruction
- DECODE instruction: ADD, SUB, XOR, etc
- READ operands (Ra, Rb) from Register File;
- PERFORM indicated operation;
- WRITE result back into Register File (Rc).

Instruction Fetch/Decode

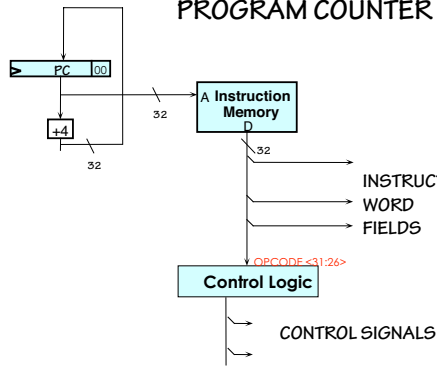• Use a counter to FETCH the next instruction:
PROGRAM COUNTER (PC)




- use PC as memory address
- add 4 to PC, load new value at end of cycle
- fetch instruction from memory
- use some instruction fields directly (register numbers, 16-bit constant)
- use bits <31:26> to generate controls

ALU Op Data Path



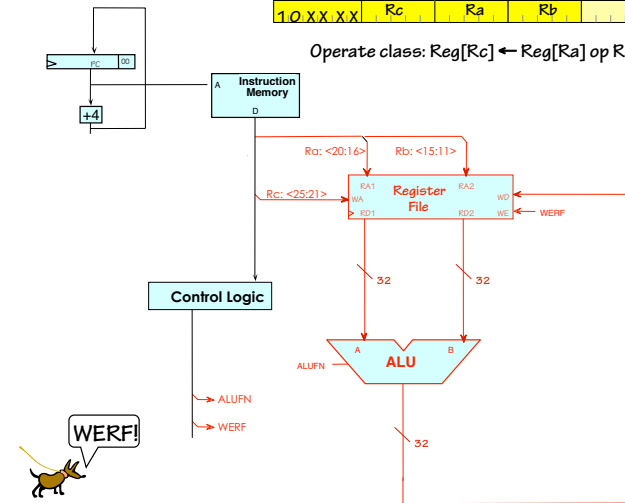
Operate class: $Reg[Rc] \leftarrow Reg[Ra] \text{ op } Reg[Rb]$



ALU Operations (w/constant)



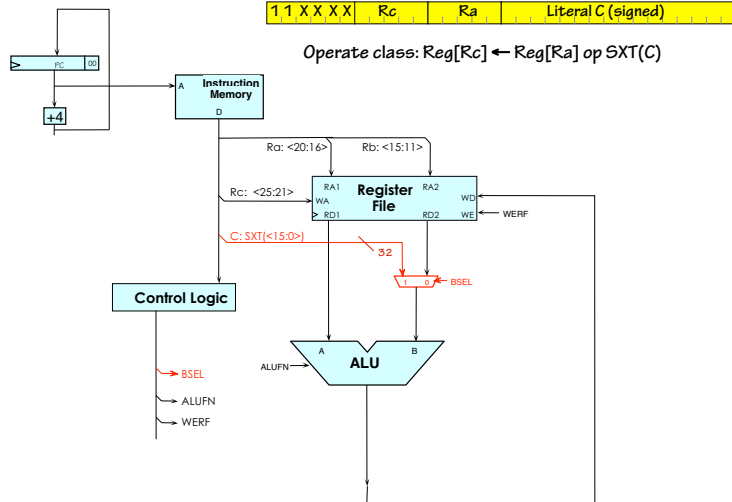
Operate class: $Reg[Rc] \leftarrow Reg[Ra] \text{ op } SXT(C)$




Load Instruction



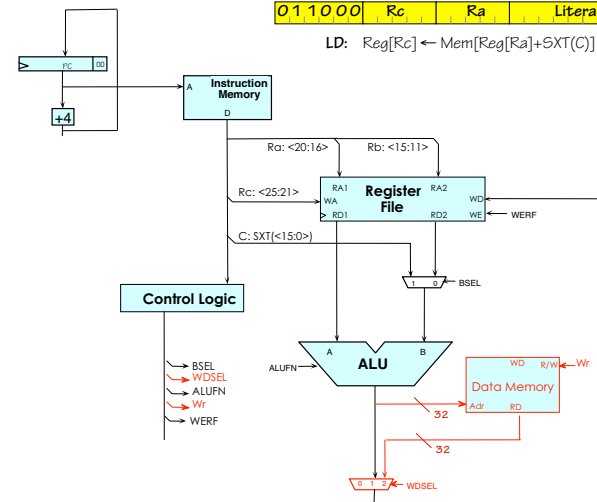
LD: $Reg[Rc] \leftarrow Mem[Reg[Ra] + SXT(C)]$




Store Instruction

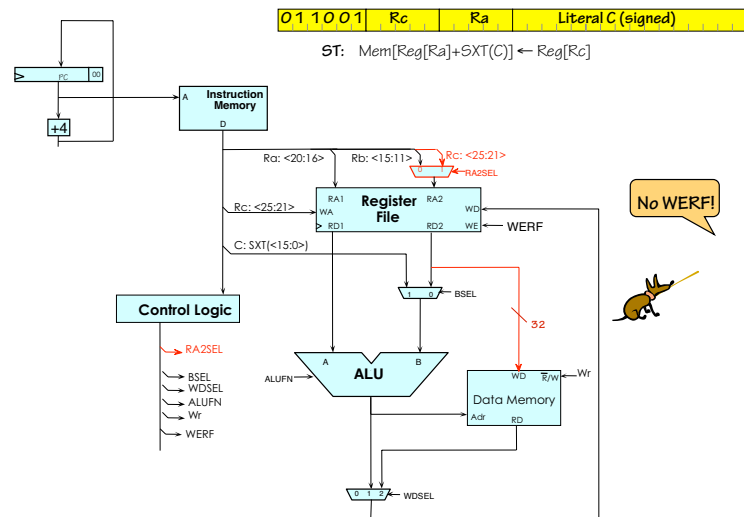


JMP Instruction

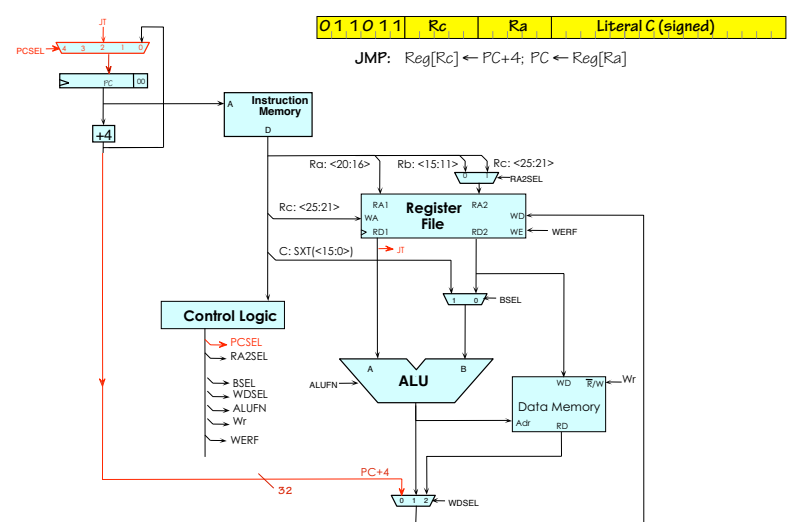

BEQ/BNE Instructions

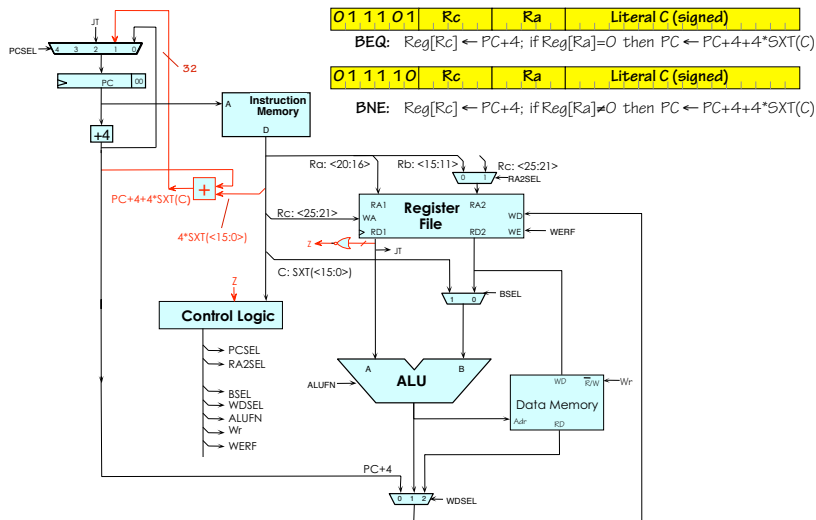

Load Relative Instruction

 

Hey, WAIT A MINUTE. What's Load Relative good for anyway???

- Code is "PURE", i.e. READ-ONLY; and stored in a "PROGRAM" region of memory;
- Data is READ-WRITE, and stored either
 - On the STACK (local); or
 - In some GLOBAL VARIABLE region; or
 - In a global storage HEAP.

So why an instruction designed to load data that's "near" the instruction???


Addresses & other large constants

```

C:   X = X * 123456;

BETA:
LD(X, r0)
LDR(c1, r1)
MUL(r0, r1, r0)
ST(r0, X)
...
c1:  LONG(123456)
    
```

LDR Instruction

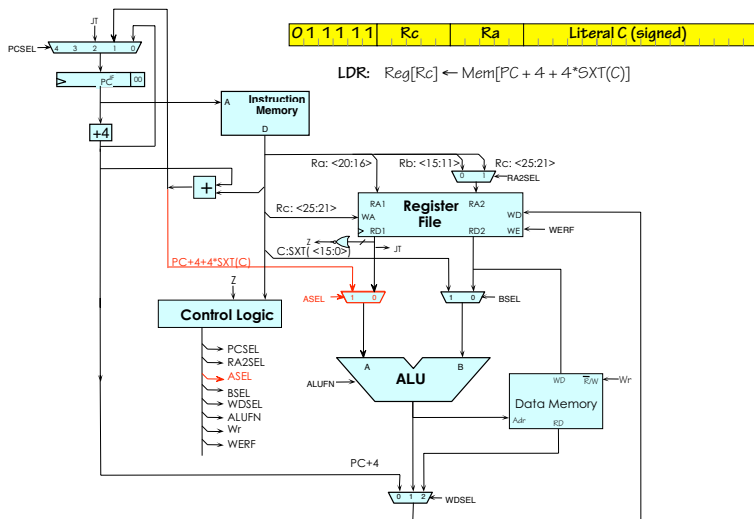

Exceptions

What if something BAD happens?

- Execution of an illegal op-code
- Reference to non-existent memory
- Divide by zero

Or, maybe, just something unanticipated...

- User hits a key
- A packet comes in via the network

GOAL: handle all these cases (and more) in SOFTWARE:

- Treat each such case as an (implicit) procedure call...
- Procedure handles problem, returns to interrupted program.
- *TRANSPARENT* to interrupted program!
- Important added capability: handlers for certain errors (illegal op-codes) can extend instruction set using software (Lab 7!).

Exception Processing

Plan:

- Interrupt running program
- Invoke exception handler (like a procedure call)
- Return to continue execution.

We'd like **RECOVERABLE INTERRUPTS** for

- Synchronous events, generated by CPU or system FAULTS (eg, Illegal Instruction, divide-by-0, illegal mem address) TRAPS & system calls (eg, read-a-character)
- Asynchronous events, generated by I/O (eg, key struck, packet received, disk transfer complete)

KEY: **TRANSPARENCY** to interrupted program.

- Most difficult for asynchronous interrupts

Implementation...

How exceptions work:

- Don't execute current instruction
- Instead fake a "forced" procedure call
 - save current PC (actually current PC + 4)
 - load PC with *exception vector*
 - 0x4 for synch. exception, 0xB for asynch. exceptions

Question: where to save current PC + 4?

- Our approach: reserve a register (R30, aka XP)
- Prohibit user programs from using XP. Why?

Example: DIV unimplemented

```
LD (R31, A, R0)
LD (R31, B, R1)
DIV (R0, R1, R2)
ST (R2, C, R31)
```


Forced by hardware

IllOp:
PUSH (XP)

Fetch inst. at Mem[Reg[XP]-4]
check for DIV opcode, get reg numbers
perform operation in SW, fill result reg

POP (XP)
JMP (XP)

Exceptions

 


Control Logic

	OP	OPC	LD	ST	JMP	BEQ	BNE	LDR	IlloP	IRQ
ALUFN	F(op)	F(op)	"+"	"+"	--	--	--	"A"	--	--
WERF	1	1	1	0	1	1	1	1	1	1
BSEL	0	1	1	1	--	--	--	--	--	--
WDSEL	1	1	2	--	0	0	0	2	0	0
WR	0	0	0	1	0	0	0	0	0	0
RA2SEL	0	--	--	1	--	--	--	--	--	--
PCSEL	0	0	0	0	2	Z ? 1 : 0	Z ? 0 : 1	0	3	4
ASEL	0	0	0	0	--	--	--	1	--	--
WASEL	0	0	0	--	0	0	0	0	1	1

Implementation choices:

- ROM indexed by opcode, external branch & trap logic
- PLA
- "random" logic (eg, standard cell gates)

Beta: Our "Final Answer"

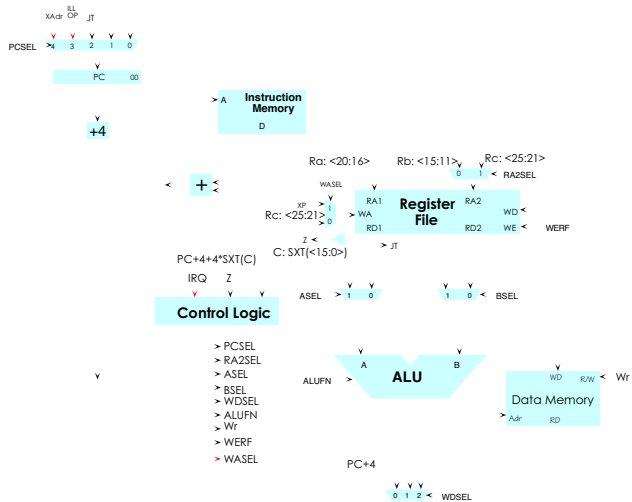

Next Time: Tackling the Memory Bottleneck

