

MIT OpenCourseWare
<http://ocw.mit.edu>

6.013/ESD.013J Electromagnetics and Applications, Fall 2005

Please use the following citation format:

Markus Zahn, Erich Ippen, and David Staelin, *6.013/ESD.013J Electromagnetics and Applications, Fall 2005*. (Massachusetts Institute of Technology: MIT OpenCourseWare). <http://ocw.mit.edu> (accessed MM DD, YYYY). License: Creative Commons Attribution-Noncommercial-Share Alike.

Note: Please use the actual date you accessed this material in your citation.

For more information about citing these materials or our Terms of Use, visit:
<http://ocw.mit.edu/terms>

Massachusetts Institute of Technology
 Department of Electrical Engineering and Computer Science
 6.013 Electromagnetics and Applications


Problem Set #7
 Fall Term 2005

Issued: 10/25/05
 Due: 11/2/05

Suggested Reading Assignment: Sections 5.2, 10.6.4

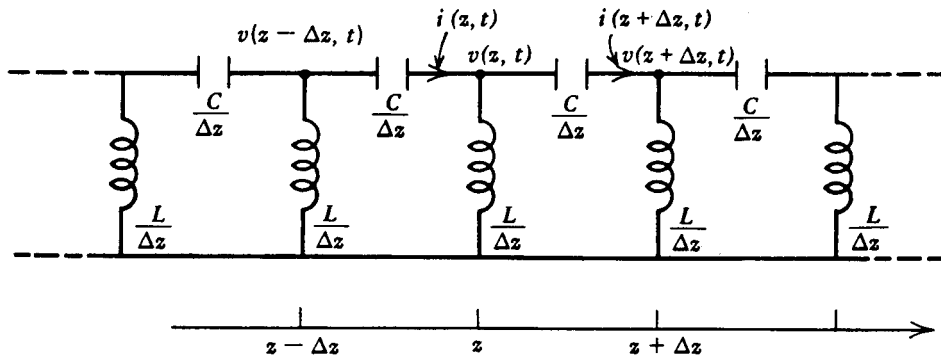Problem 7.1

An unusual type of distributed system is formed by series capacitors and shunt inductors.




- (a) What are the governing partial differential equations relating the voltage and current?
Hint: Review Lecture 10, pp. 2-3 (Section I.C.)
- (b) What is the dispersion relation between ω and k for signals of the form $e^{j(\omega t - kz)}$?
- (c) What are the group ($d\omega/dk$) and phase velocities (ω/k) of the waves? Why are such systems called “backward wave”?
- (d) A voltage $V_0 \cos \omega t$ is applied at $z = -l$ with the $z = 0$ end short circuited. What are the voltage and current distributions along the line?
- (e) What are the resonant frequencies of the system?

Problem 8.5 in *Electromagnetic Field Theory: A Problem Solving Approach*, by Markus Zahn, 1987. Used with permission.

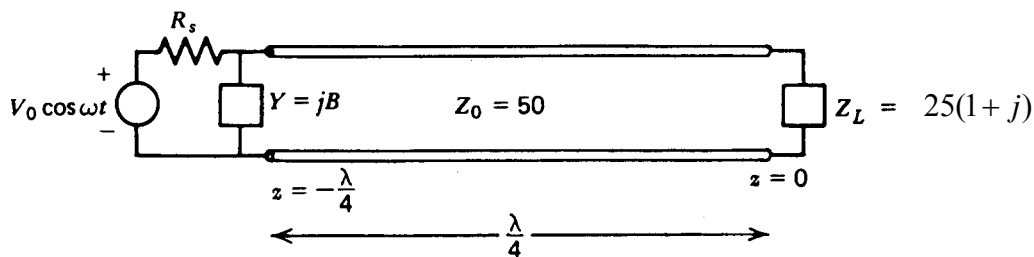Problem 7.2

For the transmission line shown, the length of the line is $\frac{1}{4}$ wavelength ($\lambda/4$) at the driving frequency ω of the voltage source.




- Find the values of lumped reactive admittance $Y = jB$ and non-zero source resistance R_s that maximizes the power delivered by the source. (**Hint:** Do not use the Smith chart.)
- If the lumped reactive admittance $Y = jB$ is made from a short circuited transmission line of length l and characteristic impedance $Z_0 = 50\Omega$, what is l in terms of wavelength λ , i.e., $l = a\lambda$, what is a ?
- What is the time-average power dissipated in the load?
- The driving frequency of the voltage source is now doubled. What is the transmission line length in terms of wavelengths λ at the frequency 2ω ? Repeat (a) to (c).

Adapted from Problem 8.19 in *Electromagnetic Field Theory: A Problem Solving Approach*, by Markus Zahn, 1987. Used with permission.

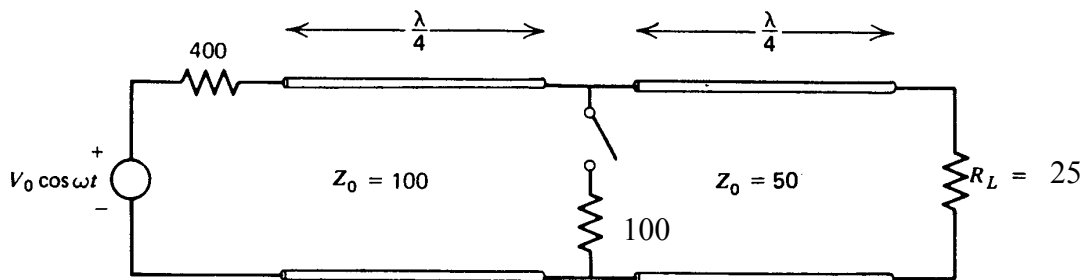Problem 7.3

- Find the time-average power delivered by the source for the transmission line system shown below when the switch is open or closed. (**Hint:** Do not use the Smith chart.)



- For each switch position, what is the time average power dissipated in the load resistor R_L ?

Adapted from Problem 8.20 in *Electromagnetic Field Theory: A Problem Solving Approach*, by Markus Zahn, 1987. Used with permission.

Problem 7.4

A 100-ohm TEM transmission line operating at frequency f is terminated with a load consisting of a 100-ohm resistor in series with an inductor having a reactance of $100j$, as illustrated. Additional details and values are shown in the figures.

a) In terms of the complex reflection coefficient Γ_L of the load, what fraction A of the power incident upon the load is reflected?

b) For this load what is the numerical value of the complex reflection coefficient $\Gamma_L = a + jb$?

c) At what fraction of a wavelength $q = D/\lambda$ (and in terms of β , see figure), is the distance D from the load of the first point where $Z(z)$ is purely real?*

d) To match this load a quarter-wave transformer is inserted at the first point where $Z(z)$ is purely real. In terms of K , what should be the characteristic impedance Z_T of the quarter-wave transformer (see figure)?

e) What is K ?

f) Find another set of values for q , K and Z_T that allow this load to be matched with a quarter-wave transformer with Z_T real.

***Hint** for part (c): Use Smith Chart given below.

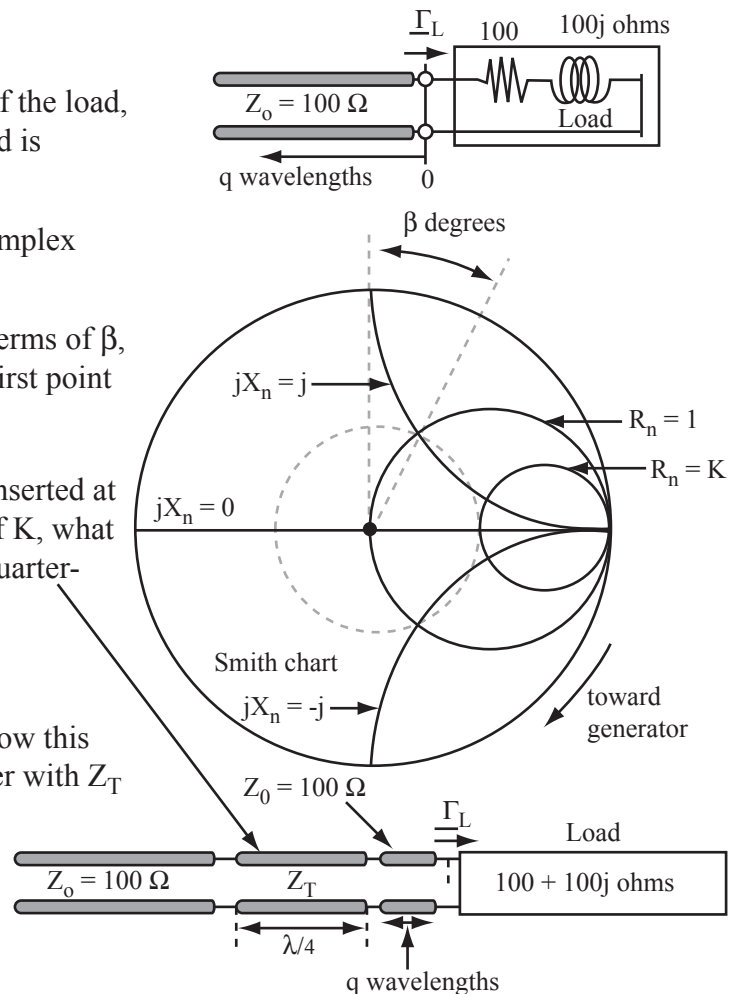


Image by MIT OpenCourseWare.

The Complete Smith Chart

Black Magic Design

