

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.013/ESD.013J Electromagnetics and Applications, Fall 2005

Please use the following citation format:

Markus Zahn, *6.013/ESD.013J Electromagnetics and Applications, Fall 2005*. (Massachusetts Institute of Technology: MIT OpenCourseWare). <http://ocw.mit.edu> (accessed MM DD, YYYY). License: Creative Commons Attribution-Noncommercial-Share Alike.

Note: Please use the actual date you accessed this material in your citation.

For more information about citing these materials or our Terms of Use, visit:  
<http://ocw.mit.edu/terms>

## Lecture 10 - Transmission Lines

Prof. Markus Zahn

October 13, 2005

## I. Transmission Line Equations

## A. Parallel Plate Transmission Line

$\vec{E}$  must be perpendicular to the electrodes and  $\vec{H}$  must be tangential, so

$$\vec{E} = E_x(z, t)\vec{i}_x$$

$$\vec{H} = H_y(z, t)\vec{i}_y$$

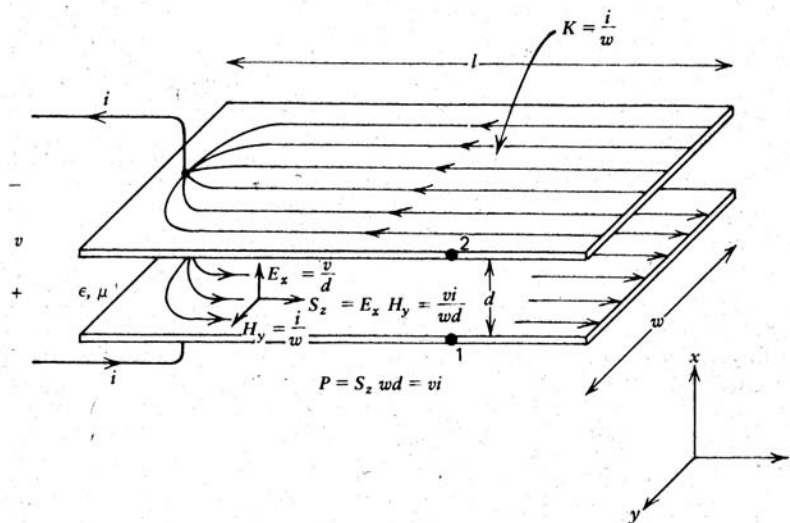


Figure 8-1 The simplest transmission line consists of two parallel perfectly conducting plates a small distance  $d$  apart.

From *Electromagnetic Field Theory: A Problem Solving Approach*, by Markus Zahn, 1987. Used with permission.

$$\nabla \times \vec{E} = -\mu \frac{\partial \vec{H}}{\partial t} \Rightarrow \frac{\partial E_x}{\partial z} = -\mu \frac{\partial H_y}{\partial t}$$

$$\nabla \times \vec{H} = \epsilon \frac{\partial \vec{E}}{\partial t} \Rightarrow \frac{\partial H_y}{\partial z} = -\epsilon \frac{\partial E_x}{\partial t}$$

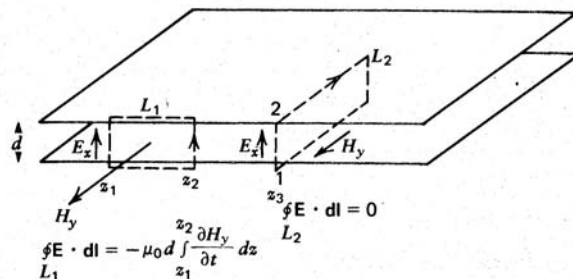


Figure 8-2 The potential difference measured between any two arbitrary points at different positions  $z_1$  and  $z_2$  on the transmission line is not unique—the line integral  $L_1$  of the electric field is nonzero since the contour has magnetic flux passing through it. If the contour  $L_2$  lies within a plane of constant  $z$  such as at  $z_3$ , no magnetic flux passes through it so that the voltage difference between the two electrodes at the same value of  $z$  is unique.

From *Electromagnetic Field Theory: A Problem Solving Approach*, by Markus Zahn, 1987. Used with permission.

$$v(z, t) = \int_1^2 \bar{E} \cdot d\bar{l} = E_x(z, t)d$$

$z = \text{constant}$

$$i(z, t) = K_z(z, t)w = H_y(z, t)w$$

$$\frac{\partial v}{\partial z} = -L \frac{\partial i}{\partial t} \quad L = \frac{\mu d}{w} \text{ henries / meter} \quad \text{Inductance per unit length}$$

$$\frac{\partial i}{\partial z} = -C \frac{\partial v}{\partial t} \quad C = \frac{\epsilon w}{d} \text{ farads / meter} \quad \text{Capacitance per unit length}$$

$$LC = \frac{\mu d}{w} \frac{\epsilon w}{d} = \mu\epsilon = \frac{1}{c^2}$$

### B. Transmission Line Structures

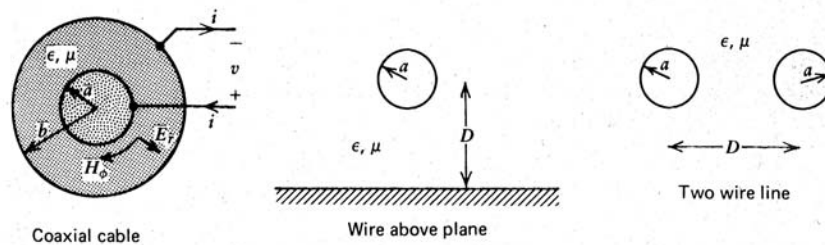


Figure 8-3 Various types of simple transmission lines.

From *Electromagnetic Field Theory: A Problem Solving Approach*, by Markus Zahn, 1987. Used with permission.

#### EXAMPLE 8-1 THE COAXIAL TRANSMISSION LINE

Consider the coaxial transmission line shown in Figure 8-3 composed of two perfectly conducting concentric cylinders of radii  $a$  and  $b$  enclosing a linear medium with permittivity  $\epsilon$  and permeability  $\mu$ . We solve for the transverse dependence of the fields as if the problem were static, independent of time. If the voltage difference between cylinders is  $v$  with the inner cylinder carrying a total current  $i$  the static fields are

$$E_r = \frac{v}{r \ln(b/a)}, \quad H_\phi = \frac{i}{2\pi r}$$

From *Electromagnetic Field Theory: A Problem Solving Approach*, by Markus Zahn, 1987. Used with permission.

The surface charge per unit length  $q$  and magnetic flux per unit length  $\lambda$  are

$$q = \epsilon E_r(r=a)2\pi a = \frac{2\pi\epsilon v}{\ln(b/a)}$$

$$\lambda = \int_a^b \mu H_\phi dr = \frac{\mu i}{2\pi} \ln \frac{b}{a}$$

so that the capacitance and inductance per unit length of this structure are

$$C = \frac{q}{v} = \frac{2\pi\epsilon}{\ln(b/a)}, \quad L = \frac{\lambda}{i} = \frac{\mu}{2\pi} \ln \frac{b}{a}$$

where we note that as required

$$LC = \epsilon\mu$$


Substituting  $E_r$  and  $H_\phi$  into (12) yields the following transmission line equations:

$$\frac{\partial E_r}{\partial z} = -\mu \frac{\partial H_\phi}{\partial t} \Rightarrow \frac{\partial v}{\partial z} = -L \frac{\partial i}{\partial t}$$

$$\frac{\partial H_\phi}{\partial z} = -\epsilon \frac{\partial E_r}{\partial t} \Rightarrow \frac{\partial i}{\partial z} = -C \frac{\partial v}{\partial t}$$

From *Electromagnetic Field Theory: A Problem Solving Approach*, by Markus Zahn, 1987. Used with permission.
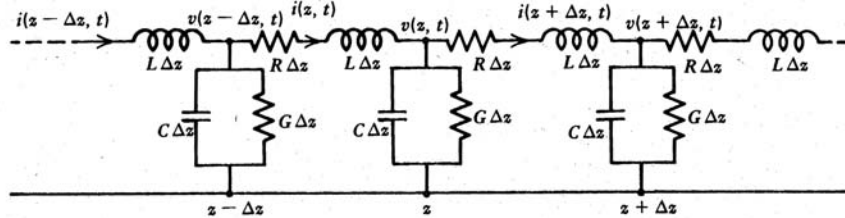
### C. Distributed Circuit Representation with Losses



$$v(z, t) - v(z + \Delta z, t) = L \Delta z \frac{\partial}{\partial t} i(z + \Delta z, t) + i(z + \Delta z, t) R \Delta z$$

$$i(z, t) - i(z + \Delta z, t) = C \Delta z \frac{\partial}{\partial t} v(z, t) + G \Delta z v(z, t)$$

Figure 8-5 Distributed circuit model of a transmission line including small series and shunt resistive losses.

From *Electromagnetic Field Theory: A Problem Solving Approach*, by Markus Zahn, 1987. Used with permission.

$$i(z, t) - i(z + \Delta z, t) = C \Delta z \frac{\partial v(z, t)}{\partial t} + G \Delta z v(z, t)$$

$$v(z, t) - v(z + \Delta z, t) = L \Delta z \frac{\partial i(z + \Delta z, t)}{\partial t} + i(z + \Delta z, t) R \Delta z$$

$$\lim_{\Delta z \rightarrow 0} \frac{i(z + \Delta z, t) - i(z, t)}{\Delta z} = \frac{\partial i}{\partial z} = -C \frac{\partial v}{\partial t} - Gv$$

$$\lim_{\Delta z \rightarrow 0} \frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = \frac{\partial v}{\partial z} = -L \frac{\partial i}{\partial t} - iR$$

$R$  is the series resistance per unit length, measured in ohms/meter, and  $G$  is the shunt conductance per unit length, measured in siemens/meter.

If the line is lossless ( $R = G = 0$ ), we have the Telegrapher's equations:

$$\begin{aligned}\frac{\partial i}{\partial z} &= -C \frac{\partial v}{\partial t} \\ \frac{\partial v}{\partial z} &= -L \frac{\partial i}{\partial t}\end{aligned}$$

Including loss, Poynting's theorem for the circuit equivalent form is:

$$\begin{aligned}v \cdot \left| \frac{\partial i}{\partial z} \right. &= -C \frac{\partial v}{\partial t} - Gv \\ i \cdot \left| \frac{\partial v}{\partial z} \right. &= -L \frac{\partial i}{\partial t} - iR \\ \text{Add: } v \frac{\partial i}{\partial z} + i \frac{\partial v}{\partial z} &= \frac{\partial(vi)}{\partial z} = -\frac{\partial}{\partial t} \left[ \frac{1}{2} C v^2 + \frac{1}{2} L i^2 \right] - Gv^2 - i^2 R\end{aligned}$$

D. Wave Equation (Lossless,  $R = 0, G = 0$ )

$$\begin{aligned}\frac{\partial}{\partial t} \left| \frac{\partial i}{\partial z} \right. &= -C \frac{\partial v}{\partial t} \Rightarrow \frac{\partial^2 i}{\partial z \partial t} = -C \frac{\partial^2 v}{\partial t^2} \\ \frac{\partial}{\partial z} \left| \frac{\partial v}{\partial z} \right. &= -L \frac{\partial i}{\partial t} \Rightarrow \frac{\partial^2 i}{\partial z \partial t} = -\frac{1}{L} \frac{\partial^2 v}{\partial z^2} \\ -\frac{1}{L} \frac{\partial^2 v}{\partial z^2} &= -C \frac{\partial^2 v}{\partial t^2} \Rightarrow \underbrace{\frac{\partial^2 v}{\partial z^2} = LC \frac{\partial^2 v}{\partial t^2} = \frac{1}{c^2} \frac{\partial^2 v}{\partial t^2}}_{\text{Wave equation}}\end{aligned}$$

## II. Sinusoidal Steady State

### A. Complex Amplitude Notation

$$\begin{aligned}v(z, t) &= \text{Re} [\hat{v}(z) e^{j\omega t}] \\ i(z, t) &= \text{Re} [\hat{i}(z) e^{j\omega t}]\end{aligned}$$

Substitute into the wave equation:

$$\begin{aligned}\frac{\partial^2 v}{\partial z^2} &= \frac{1}{c^2} \frac{\partial^2 v}{\partial t^2} \Rightarrow \frac{d^2 \hat{v}}{dz^2} = -\frac{\omega^2}{c^2} \hat{v}(z), \text{ let } k = \frac{\omega}{c} \\ \frac{d^2 \hat{v}}{dz^2} + k^2 \hat{v} &= 0 \Rightarrow \hat{v}(z) = \hat{V}_+ e^{-jkz} + \hat{V}_- e^{+jkz} \\ \frac{d\hat{v}}{dz} &= -Lj\omega \hat{i} \Rightarrow \hat{i}(z) = -\frac{1}{Lj\omega} \left( -jk\hat{V}_+ e^{-jkz} + jk\hat{V}_- e^{+jkz} \right) \\ \frac{k}{\omega} = \frac{\cancel{\omega}}{c\cancel{\omega}} &= \sqrt{LC} \Rightarrow \frac{k}{\omega L} = \frac{\sqrt{LC}}{L} = \sqrt{\frac{C}{L}} = Y_0 \text{ is the Line Admittance} \\ Z_0 &= \frac{1}{Y_0} = \sqrt{\frac{L}{C}} \text{ is the Line Impedance} \\ \hat{i}(z) &= Y_0 \left( \hat{V}_+ e^{-jkz} - \hat{V}_- e^{+jkz} \right)\end{aligned}$$

$$\hat{v}(z) = \hat{V}_+ e^{-jkz} + \hat{V}_- e^{+jkz}$$

$$v(z, t) = \text{Re} \left[ \hat{V}_+ e^{j(\omega t - kz)} + \hat{V}_- e^{j(\omega t + kz)} \right]$$

$$i(z, t) = \text{Re} Y_0 \left[ \hat{V}_+ e^{j(\omega t - kz)} - \hat{V}_- e^{j(\omega t + kz)} \right]$$

$$k = \frac{\omega}{c} = \omega \sqrt{LC} = \omega \sqrt{\epsilon \mu}$$

B. Short Circuited Line ( $v(z = 0, t) = 0, v(z = -l, t) = V_0 \cos(\omega t)$ )

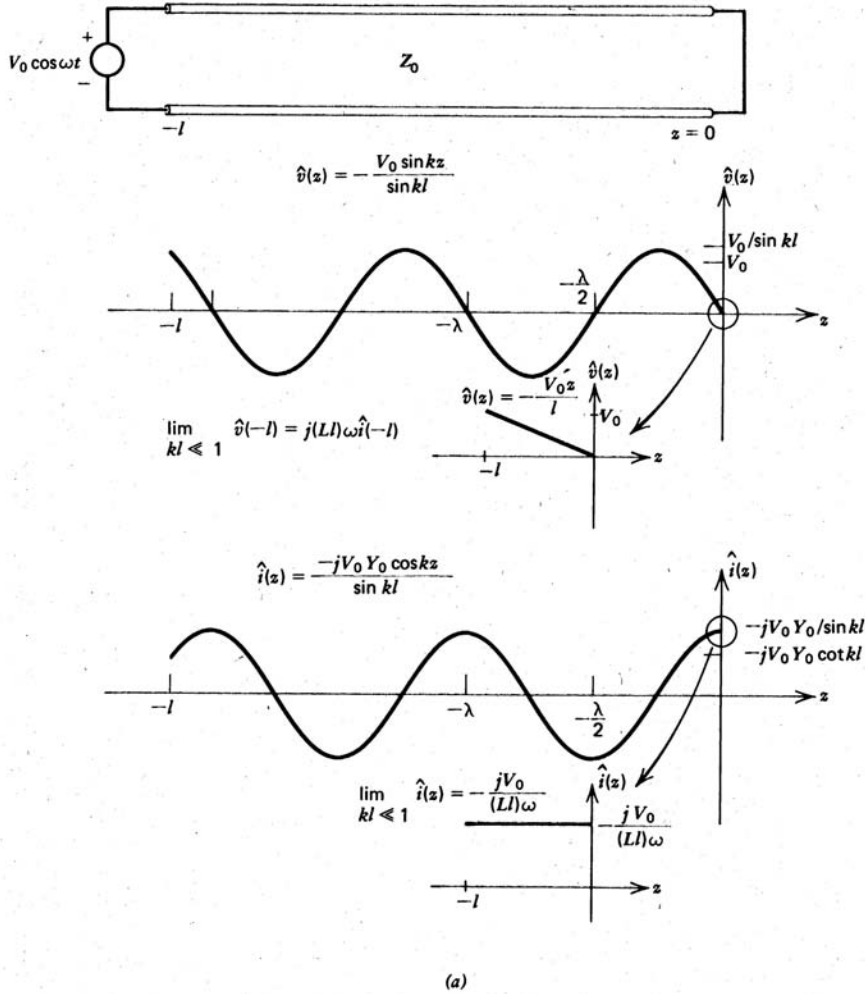


Figure 8-15 The voltage and current distributions on a (a) short circuited and (b) open circuited transmission line excited by sinusoidal voltage sources at  $z = -l$ . If the lines are much shorter than a wavelength, they act like reactive circuit elements. (c) As the frequency is raised, the impedance reflected back as a function of  $z$  can look capacitive or inductive making the transition through open or short circuits.

From *Electromagnetic Field Theory: A Problem Solving Approach*, by Markus Zahn, 1987. Used with permission.

$$\hat{v}(z) = \hat{V}_+ e^{-jkz} + \hat{V}_- e^{+jkz} \Rightarrow \hat{v}(z = 0) = 0 = \hat{V}_+ + \hat{V}_- \Rightarrow \hat{V}_+ = -\hat{V}_-$$

$$\hat{v}(z = -l) = V_0 = \hat{V}_+ e^{+jkl} + \hat{V}_- e^{-jkl} = \hat{V}_+ \left( e^{jkl} - e^{-jkl} \right)$$

$$= 2j \sin(kl) \hat{V}_+$$

$$\hat{V}_+ = -\hat{V}_- = \frac{V_0}{2j \sin(kl)}$$

$$\hat{v}(z) = \frac{V_0}{2j \sin(kl)} (e^{-jkz} - e^{+jkz}) = \frac{V_0(-2j) \sin(kz)}{2j \sin(kl)}$$

$$= -\frac{V_0 \sin(kz)}{\sin(kl)}$$

$$\hat{i}(z) = Y_0 (\hat{V}_+ e^{-jkz} - \hat{V}_- e^{+jkz}) = \frac{Y_0 V_0}{2j \sin(kl)} (e^{-jkz} + e^{+jkz})$$

$$= \frac{2Y_0 V_0 \cos(kz)}{2j \sin(kl)}$$

$$= -\frac{jY_0 V_0 \cos(kz)}{\sin(kl)}$$

$$v(z, t) = \text{Re} [\hat{v}(z) e^{j\omega t}] = \text{Re} \left[ -\frac{V_0 \sin(kz)}{\sin(kl)} e^{j\omega t} \right] = -\frac{V_0 \sin(kz) \cos(\omega t)}{\sin(kl)}$$

$$i(z, t) = \text{Re} [\hat{i}(z) e^{j\omega t}] = \text{Re} \left[ -\frac{jY_0 V_0 \cos(kz)}{\sin(kl)} e^{j\omega t} \right] = \frac{Y_0 V_0 \cos(kz) \sin(\omega t)}{\sin(kl)}$$

We have resonance when  $\sin(kl) = 0 \Rightarrow kl = n\pi = \frac{\omega l}{c} \Rightarrow \omega = \omega_n \equiv \frac{n\pi c}{l}, n = 1, 2, 3, \dots$

Complex impedance:  $Z(z) = \frac{\hat{v}(z)}{\hat{i}(z)} = -jZ_0 \tan(kz)$

$$Z(z = -l) = +jZ_0 \tan(kl)$$

In the following, take  $n = 1, 2, 3, \dots$ :

$kl = n\pi$	$Z(z = -l) = 0$	short circuit
$kl = (2n - 1)\frac{\pi}{2}$	$Z(z = -l) = \infty$	open circuit
$(n - 1)\pi < kl < (2n - 1)\frac{\pi}{2}$	$Z(z = -l) = +jX, X > 0$	(positive reactance, inductive)
$(n - \frac{1}{2})\pi < kl < n\pi$	$Z(z = -l) = -jX, X > 0$	(negative reactance, capacitive)
$kl \ll 1 \Rightarrow$	$Z(z) = -jZ_0 k$ $= -j\sqrt{\frac{L}{C}} \omega \sqrt{LC}$ $= -jLZ$	$Z(z = -l) = j(Ll)$ inductive
$ kz  \ll 1$	$v(z, t) = -\frac{V_0 z}{l} \cos(\omega t) \Rightarrow$	$v(z = -l, t) = V_0 \cos(\omega t)$ $= (Ll) \frac{di}{dt}(z = -l, t)$
	$i(z, t) = \frac{V_0 Y_0}{kl} \sin(\omega t)$	$i(z = -l, t) = \frac{V_0 \sin(\omega t)}{(Ll)\omega}$

C. Open Circuited Line ( $i(z = 0, t) = 0$ )

$$\begin{aligned}
 v(z = -l, t) &= V_0 \sin(\omega t) \\
 \hat{i}(z) &= Y_0 [\hat{V}_+ e^{-jkz} - \hat{V}_- e^{+jkz}] \Rightarrow \hat{i}(z = 0) = 0 = Y_0 [\hat{V}_+ - \hat{V}_-] \Rightarrow \hat{V}_+ = \hat{V}_- \\
 \hat{v}(z = -l) &= -jV_0 = \hat{V}_+ e^{+jkl} + \hat{V}_- e^{-jkl} = \hat{V}_+ (e^{jkl} + e^{-jkl}) = 2\hat{V}_+ \cos(kl) \\
 \hat{V}_+ = \hat{V}_- &= -\frac{jV_0}{2 \cos(kl)} \\
 \hat{v}(z) &= -\frac{jV_0}{2 \cos(kl)} (e^{-jkz} + e^{+jkz}) \\
 &= -\frac{jV_0 \cdot 2 \cos(kz)}{2 \cos(kl)} \\
 &= -\frac{jV_0 \cos(kz)}{\cos(kl)} \\
 \hat{i}(z) &= -\frac{jY_0 V_0}{2 \cos(kl)} (e^{-jkz} - e^{+jkz}) \\
 &= \frac{(-jY_0 V_0)(-2j) \sin(kz)}{2 \cos(kl)} \\
 &= -\frac{Y_0 V_0 \sin(kz)}{\cos(kl)}
 \end{aligned}$$

$$v(z, t) = \text{Re} [\hat{v}(z) e^{j\omega t}] = \frac{V_0 \cos(kz)}{\cos(kl)} \sin(\omega t)$$

$$i(z, t) = \text{Re} [\hat{i}(z) e^{j\omega t}] = \frac{-V_0 Y_0}{\cos(kl)} \sin(kz) \cos(\omega t)$$

$$\text{Resonance: } \cos(kl) = 0 \Rightarrow (kl) = (2n - 1) \frac{\pi}{2}, n = 1, 2, 3, \dots$$

$$\omega_n = \frac{(2n - 1) \frac{\pi}{2}}{2l}$$

Complex Impedance

$$Z(z) = \frac{\hat{v}(z)}{\hat{i}(z)} = Z_0 j \cot(kz)$$

$$Z(z = -l) = -jZ_0 \cot(kl)$$

$$kl \ll 1 \Rightarrow v(z, t) = V_0 \sin(\omega t)$$

$$i(z, t) = -V_0 Y_0 kz \cos(\omega t)$$

$$i(z = -l, t) = (Cl)\omega V_0 \cos(\omega t) = (Cl) \frac{dv}{dt}(z = -l, t)$$



## Open circuited line

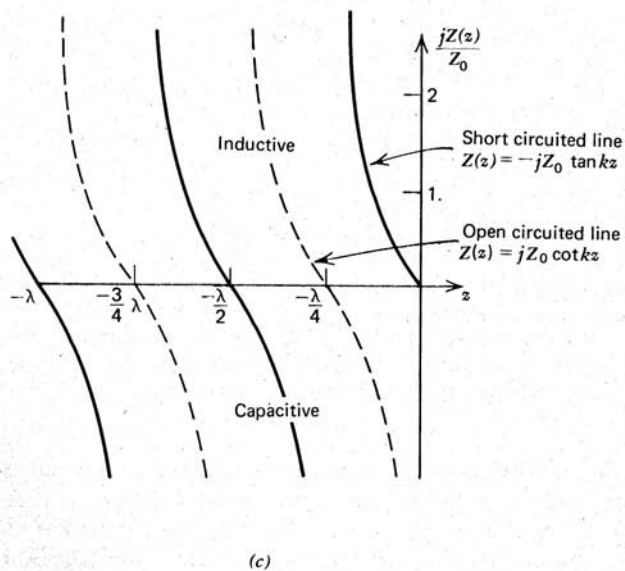
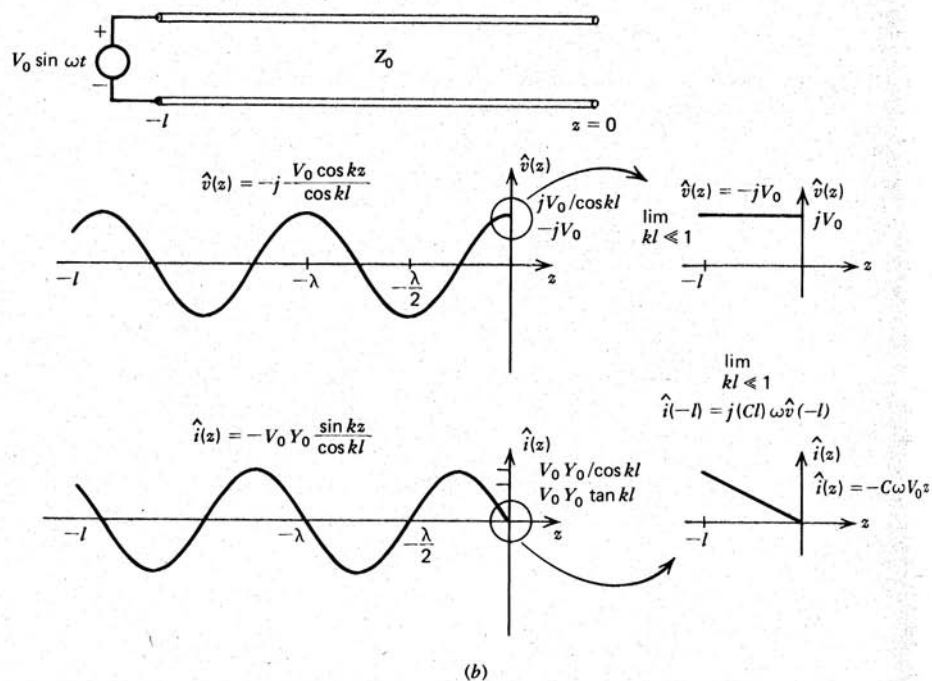


Figure 8-15

From *Electromagnetic Field Theory: A Problem Solving Approach*, by Markus Zahn, 1987. Used with permission.

Impedance for short and open circuited wires