

MASSACHUSETTS INSTITUTE OF TECHNOLOGY
6.071 Introduction to Electronics, Signals and Measurement
Spring 2006

Laboratory 16: Diodes. Signal conditioning

Exercise 1.


Use the I - V instrument to measure the I - V characteristics of a diode from your labkit. The zoom feature will give you the opportunity to investigate in detail all regions of the curve.

Exercise 2.

Build and test a **full wave rectifier** circuit. For input use the function generator to create a sinusoidal signal with an amplitude of 2.5 Volts and a frequency of 60 Hz. Increase the frequency to 1kHz, 10kHz, 50kHz and observe the resulting output.

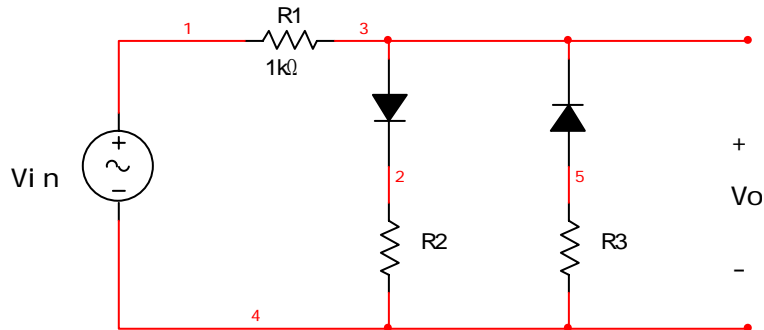Exercise 3.

Next let's built, analyze and test the following circuit



This circuit is called waveform clipper.

Resistor R1 is called the current limiting resistor since it limits the current through the diodes.


What is the role of resistors R2 and R3?

Use your function generator to create a triangular wave with an amplitude of 2.5 Volts. Measure the output voltage V_o with the oscilloscope and draw its form below. You may use a variable resistor in the place of R2 and R3 and observe the output as you trim the resistors.

Exercise 4.


Diode logic gates.

Built and test the following circuits

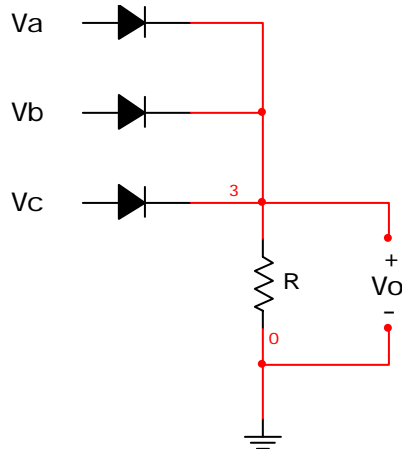

Determine the output for the following values for the voltages Va, Vb and Vc. This circuit performs the logic operation OR

Va	Vb	Vc	Vo
5V	5V	5V	
5V	0V	5V	
0V	0V	5V	

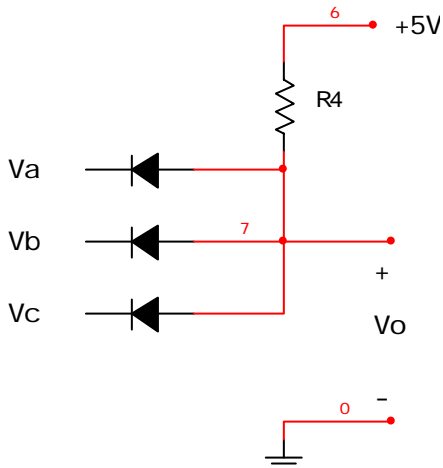


Determine the output for the following values for the voltages Va, Vb and Vc. This circuit performs the logic operation AND

Va	Vb	Vc	Vo
5V	5V	5V	
5V	0V	5V	
0V	0V	5V	

Voltage regulator

Start this experiment and complete the analysis for Monday.

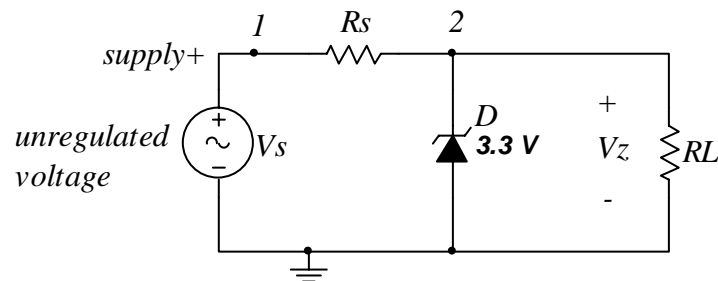The Zener diode with its well defined breakdown voltage may be used for building a very effective voltage regulator. In this exercise we will construct and test a voltage regulator circuit.



The supply is able to provide a maximum current of 1.5A, and the Zener diode has an effective resistance of 30Ω .

Using $R_s \sim 500\Omega$ and $R_L \sim 10k\Omega$ build the above circuit. From the class web site download the instrument called **ZenerRegulator**. This instrument controls the variable power supply of your ELVIS unit. Make the following connections to your protoboard.

Node 1: Connected to ACH1 (measures the unregulated voltage V_s)

Node 2: Connected to ACH2 (measures the regulated voltage V_z)

Run your instrument and observe the response of the circuit (regulated voltage V_z) as the unregulated voltage V_s is varied. Try adding noise to V_s and observe V_z .

Note the loading effect of this voltage regulator circuit. As V_s gets larger what is the max V_z across the load?

Given the maximum V_z and the diode's effective resistance calculate the maximum current through the diode I_z . What is the maximum current I_s ?