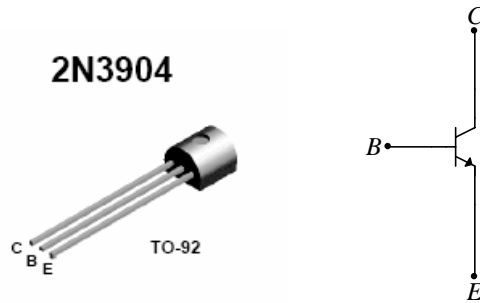


MASSACHUSETTS INSTITUTE OF TECHNOLOGY
6.071 Introduction to Electronics, Signals and Measurement
Spring 2006

Laboratory 19: BJT Biasing and Amplification

For our experiments we will use the 2N3904 npn BJT whose pinout is




Exercise 1.

For the circuit below calculate the Q-point assuming that the transistor has $\beta = 100$

- Find the Q-point for $R_1 = 20k\Omega$, $R_2 = 5k\Omega$, $R_C = 3k\Omega$, $R_E = 1k\Omega$, $V_{CC} = 10V$

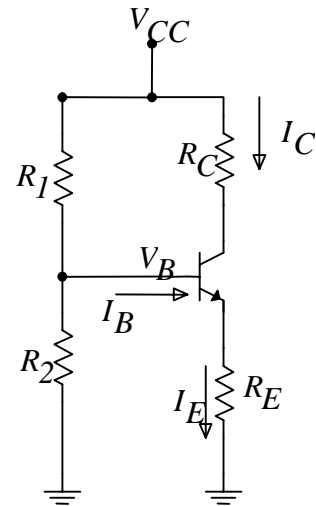
- For $R_1 = 20k\Omega$, $R_2 = 5k\Omega$, $R_E = 1k\Omega$, $V_{CC} = 10V$ determine R_C so that the collector-emitter voltage is $V_{CE} = V_{CC} / 2$



- For $R_1 = 20k\Omega$, $R_2 = 5k\Omega$, $R_E = 1k\Omega$, $V_{CC} = 10V$, determine resistor R_C so that the transistor enters saturation.

Experiment 1.

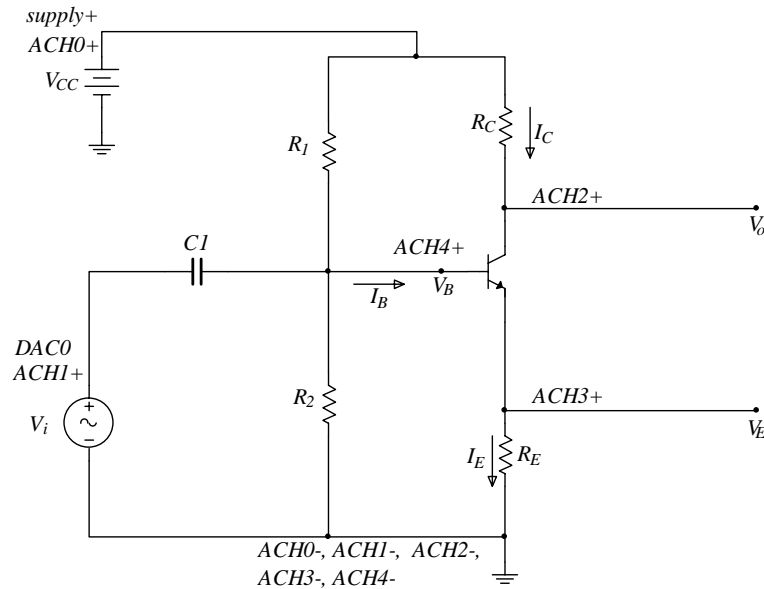Here we will build and test the common-emitter amplifier circuit shown below.



Build the circuit with $R_1 = 20k\Omega$, $R_2 = 5k\Omega$, $R_C = 5k\Omega$, $R_E = 1k\Omega$, $V_{CC} = 10V$. These values should give a Q-point: $I_{CQ} = 1.3mA$, $V_{CEQ} = 2.5V$. For V_{CC} use the variable power supply and set the voltage to 10 Volts. The signal V_i is available at $DAC0$.

What value would you use for the coupling capacitor $C1$ and why?

What is the anticipated small signal gain of this amplifier?

Make the connections as indicated on the schematic and then download from the Labs section the instrument called **BJTamp.vi** and run it.

First set the amplitude and the offset of the input signal to zero. What is the measured value of I_{CQ} and V_{CEQ} ? Do they agree with the numbers given above? How close are they? Why the difference?

Now set the offset of the input signal to a non-zero value and observe the results. Compare V_B for zero and non-zero offset for the input signal. How effective is your coupling capacitor C1 in blocking the DC component in the input signal?

Take measurements for various amplitudes of V_i (0.1V – 1.5V) and record them on the table below. PtP stands for Peak to Peak. PtP=2*Amplitude


| V_i | | V_B | | V_E | | V_o | |
|-------|--------|-------|--------|-------|--------|-------|--------|
| PtP | Offset | PtP | Offset | PtP | Offset | PtP | Offset |
| 0.2 | | | | | | | |
| 0.4 | | | | | | | |
| 0.6 | | | | | | | |
| 0.8 | | | | | | | |
| 1.0 | | | | | | | |
| 1.5 | | | | | | | |

What happens to the output V_o as the amplitude of V_i increases?

Experiment 2.

Now let's modify "slightly" the circuit by adding the load resistor R_L and the output coupling capacitor $C2$ as indicated on the following schematic. Use $R_L = 5k\Omega$.

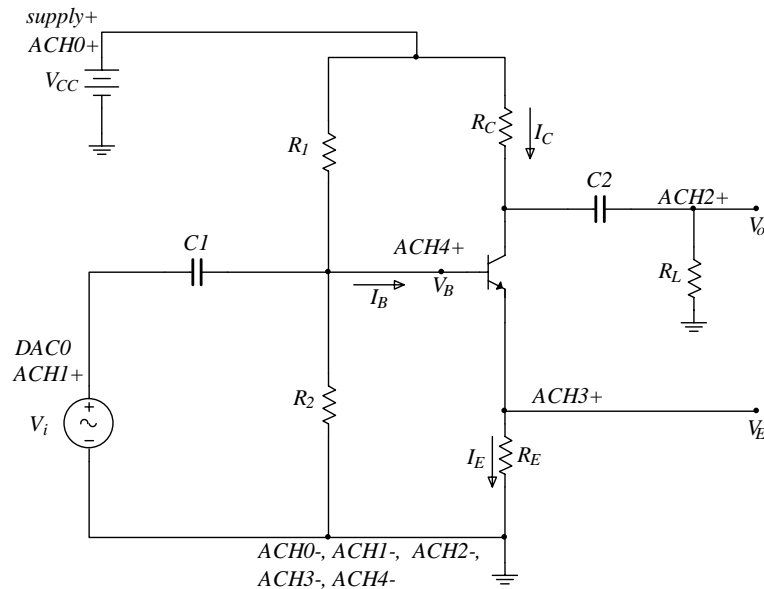R_L and $C2$ form a high pass filter thereby blocking any DC component of the voltage at the collector of the transistor. What value would you use for $C2$?



(Note now that the measurement $ACH2+$ is taken between R_L and $C2$.)

Start the instrument **BJTamp.vi** and measure the output voltage V_o for $V_i = 100mV$.

DC component of $V_o =$

Peak to peak value of $V_o =$

By comparing the above measurement with the corresponding one obtained in Experiment 1 estimate the output impedance of the device (i.e the impedance seen by the instrument that measures V_o – assume that this instrument is ideal)