

Massachusetts Institute of Technology
6.101 Analog Electronics Lab
Spring 2007
Problem Set 4
Due Wednesday, March 14, 2007

Refer to Chapters 9 of *Circuit Analysis and Design, 3rd Edition*
by Donald Neamen and *Operational Amplifier Circuits: Design and Application* for text
that supports this problem set.

Remember to use 5% standard resistor values. Assume $V_T=26\text{mV}$

- Problem 1.** Operational Amplifier Circuits: Design and Application: Problem 3.6
- Problem 2.** Operational Amplifier Circuits: Design and Application: Problem 4.11
- Problem 3.** Operational Amplifier Circuits: Design and Application: Problem 4.12
- Problem 4.** Neamen 9.45 (2nd ed: 9.31). Set all resistors equal to R (i.e. change the 2R in the two feedback resistors to R).
- Problem 5.** Neamen 9.74 (2nd ed: 9.54).