

Electrical Overview

Ref: Woud 2.3

N.B. this is a long note and repeats much of what is in the text

$$I = \frac{Q}{t} \quad Q = \text{charge} \quad C = 1 \text{ C} \quad C = 1 \text{ coul}$$

$$t = \text{time} \quad \text{min} = 60 \text{ s} \quad \text{s} = 1 \text{ s}$$

$$I = \text{current} \quad A = 1 \text{ A}$$

(2.50)

work done per unit charge = potential difference two points
aka electromotive force (EMF)

$$U = \text{volts} \quad V = 1 \text{ V}$$

$$\text{Power} = U(t) \cdot I(t) \quad 1 \text{ V} \cdot 1 \text{ A} = 1 \text{ W} \quad 1 \text{ V} \cdot 1 \text{ A} = 1 \text{ watt}$$

(2.51)

source, resistance, inductance, capacitance

resistance

resistance = R $\Omega = 1 \Omega$ ohm = 1 Ω friction in mechanical system

Ohm's law $U(t) = I(t) \cdot R$ (2.52)

power in a resistor ... $\text{Power} = U(t) \cdot I(t) = I(t)^2 \cdot R$ $1 \Omega \cdot (1 \text{ A})^2 = 1 \text{ W}$ (2.53)

inductance

mass of inertia in mechanical system

inductance = L $H = 1 \text{ H}$ henry = 1 H

$$U(t) = L \cdot \frac{d}{dt} I(t) \quad H \cdot \frac{A}{s} = 1 \text{ V} \quad \text{or ...} \quad I(t) = \int_0^t \frac{U(t)}{L} dt \quad \frac{V \cdot s}{H} = 1 \text{ A} \quad (2.54)$$

$$P = U \cdot I = L \cdot I \cdot \left(\frac{dI}{dt} \right) \quad H \cdot A \cdot \frac{A}{s} = 1 \text{ W} \quad (2.55)$$

$$\text{inductive_energy_stored} = E_{\text{ind}} = \int_0^t P(t) dt = \int_0^t L \cdot I \cdot \left(\frac{dI}{dt} \right) dt = \int_0^I L \cdot I dI \quad \int_0^I L \cdot I dI \rightarrow \frac{1}{2} \cdot I^2 \cdot L \quad (2.56)$$

$$A^2 \cdot H = 1 \text{ J}$$

capacitance

spring in mechanical system

capacitance = C $F = 1 \text{ F}$ farad = 1 F

$$I(t) = C \cdot \frac{d}{dt} U(t) \quad F \cdot \frac{V}{s} = 1 \text{ A} \quad \text{or ...} \quad U(t) = \int_0^t \frac{I(t)}{C} dt \quad \frac{A \cdot s}{F} = 1 \text{ V} \quad (2.57)$$

$$P = U \cdot I = C \cdot U \cdot \frac{d}{dt} U(t) \quad F \cdot V \cdot \frac{V}{s} = 1 \text{ W}$$

$$\text{capacitive_energy_stored} = E_{\text{cap}} = \int_0^t P(t) dt = \int_0^t C \cdot U \cdot \frac{d}{dt} U(t) dt = \int_0^U C \cdot U dU \quad \int_0^U C \cdot U dU \rightarrow \frac{1}{2} \cdot U^2 \cdot C \quad (2.58), (2.59)$$

$$V^2 \cdot F = 1 \text{ J}$$

Kirchhoff's laws

first ...

$$\text{sum_of_currents_towards_node} = 0 \quad \sum_{i=1}^{\text{number_of_currents}} [I_i(t)] = 0 \quad (2.60)$$

second ...

$$\text{sum_of_voltages_around_closed_path} = 0 \quad \text{direction specified}$$

$$\sum_{i=1}^{\text{number_of_voltages}} [U_i(t)] = 0 \quad (2.61)$$

series connection of resistance and inductance ...

$$\text{imposed ... external} \quad U(t) := U_m \cdot \cos(\omega \cdot t) \quad U_m = \text{amplitude_of_voltage} \quad V = 1 \text{ V} \quad (2.62)$$

$$\omega = \text{frequency} \quad \text{Hz} = 1 \frac{1}{\text{s}}$$

$$t = \text{time} \quad \text{min} = 60 \text{ s}$$


$$\text{resulting current assumed also harmonic} \quad I(t) := I_m \cdot \cos(\omega \cdot t - \phi) \quad I_m = \text{amplitude_of_current} \quad A = 1 \text{ amp} \quad (2.63)$$

$$\phi = \text{phase_lag_angle}$$

it is useful to represent this parameters as vectors using complex notation, where the values are represented by the real parts

$$U_z(t) := U_m \cdot \cos(\omega \cdot t) + U_m \cdot \sin(\omega \cdot t) \cdot i \quad I_z(t) := I_m \cdot \cos(\omega \cdot t - \phi) + I_m \cdot \sin(\omega \cdot t - \phi) \cdot i$$

▶ plotting set up

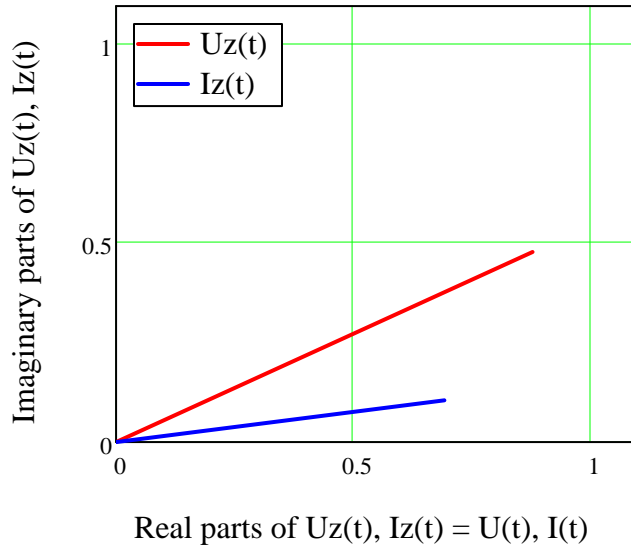

$$\text{over R voltage drop will be ...} \quad U_R(t) := R \cdot I(t) \rightarrow R \cdot I_m \cdot \cos[(-\omega) \cdot t + \phi] \quad U_R(t) = R \cdot I_m \cdot \cos(\omega \cdot t - \phi) \quad \cos(\alpha) = \cos(-\alpha)$$

$$\text{over L voltage drop will be ...} \quad U_L(t) := L \cdot \frac{d}{dt} I(t) \rightarrow L \cdot I_m \cdot \sin[(-\omega) \cdot t + \phi] \cdot \omega$$


$$L \cdot \frac{d}{dt} I(t) = -I_m \cdot \omega \cdot L \cdot \sin(\omega \cdot t - \phi) = I_m \cdot \omega \cdot L \cdot \cos\left(\frac{\pi}{2} + \omega \cdot t - \phi\right)$$


$$\cos\left(\frac{\pi}{2} + \alpha\right) \rightarrow -\sin(\alpha) \quad \text{or ...} \quad \cos\left(\frac{\pi}{2} + \alpha\right) = \cos\left(\frac{\pi}{2}\right) \cdot \cos(\alpha) - \sin\left(\frac{\pi}{2}\right) \cdot \sin(\alpha) = 0 \cdot \cos(\alpha) - 1 \cdot \sin(\alpha)$$

in complex (vector) notation ...

$$U_{zR}(t) := R \cdot I_m \cdot \cos(\omega \cdot t - \phi) + R \cdot I_m \cdot \sin(\omega \cdot t - \phi) \cdot i$$

$$U_{zL}(t) := I_m \cdot \omega \cdot L \cdot \cos\left(\frac{\pi}{2} + \omega \cdot t - \phi\right) + I_m \cdot \omega \cdot L \cdot \sin\left(\frac{\pi}{2} + \omega \cdot t - \phi\right) \cdot i$$

 plotting set up

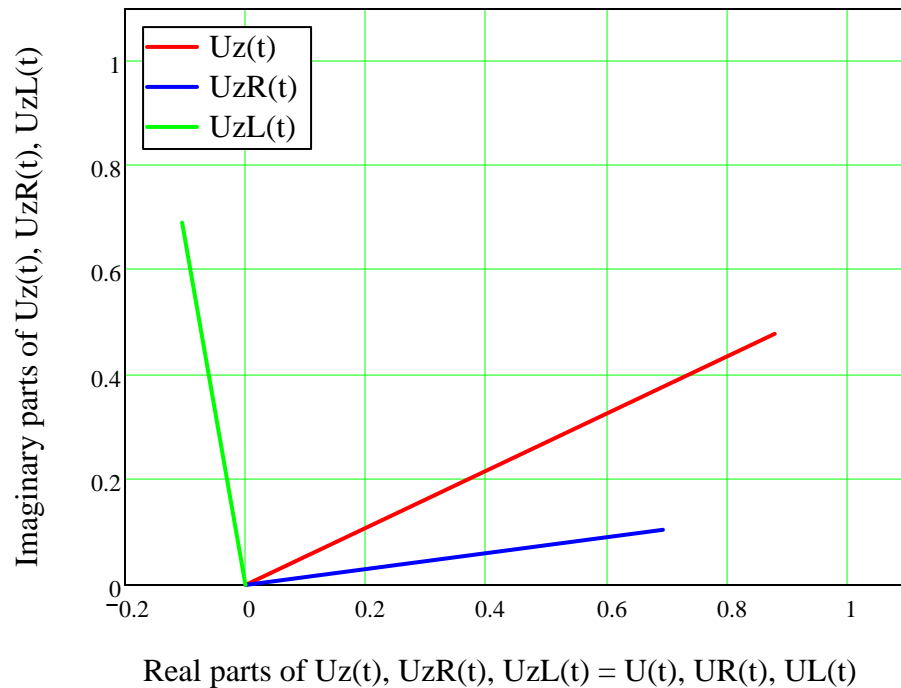

at this point these vectors are shown with two unknowns included I_m and ϕ


i.e. directions are correct relatively given ϕ and magnitudes arbitrary given I_m

Kirchoff's second law ...

$$U(t) := U_R(t) + U_L(t) \rightarrow R \cdot I_m \cdot \cos[(-\omega) \cdot t + \phi] + L \cdot I_m \cdot \sin[(-\omega) \cdot t + \phi] \cdot \omega$$

$$U_m \cdot \cos(\omega \cdot t) = R \cdot I_m \cdot \cos(\omega \cdot t - \phi) + L \cdot I_m \cdot \omega \cdot \cos\left(\frac{\pi}{2} + \omega \cdot t - \phi\right)$$

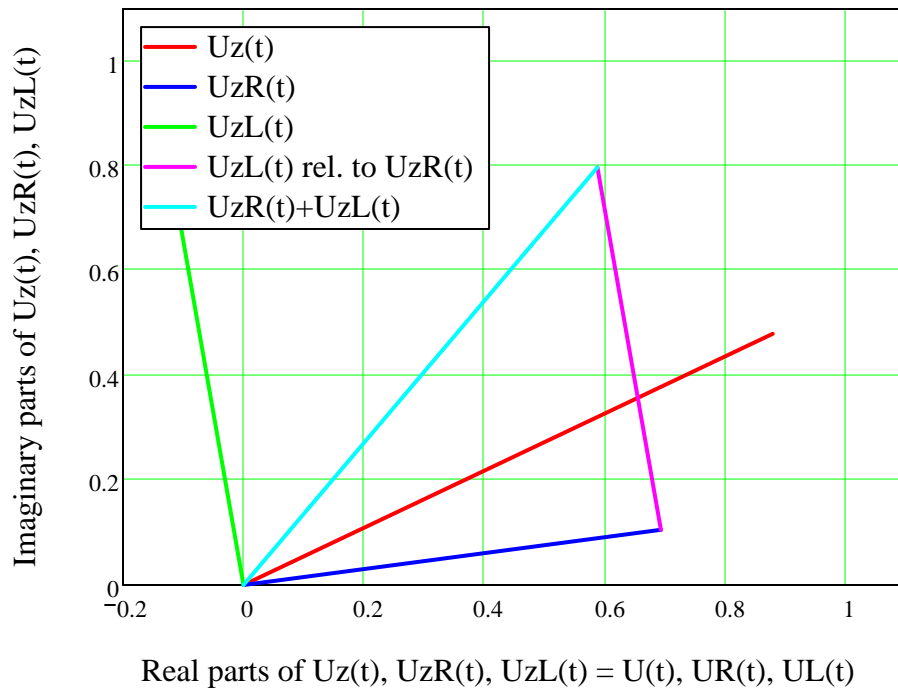this can be solved for ϕ and I_m after expanding the rhs into sines and cosines and setting $\cos = \cos$ and $\sin = \sin$
easier if think in terms of vectors



for $UzR(t) + zL(t) = Uz(t)$ magnitude and angle must be =

$$Uz(t) \rightarrow U_m \cdot \cos(\omega \cdot t) + i \cdot U_m \cdot \sin(\omega \cdot t)$$

$$U_m = \sqrt{(R \cdot I_m)^2 + (L \cdot I_m \cdot \omega)^2} = \sqrt{R^2 + (L \cdot \omega)^2} \cdot I_m$$

$$UzR(t) \rightarrow R \cdot I_m \cdot \cos[(-\omega) \cdot t + \phi] - i \cdot R \cdot I_m \cdot \sin[(-\omega) \cdot t + \phi]$$

$$UzL(t) \rightarrow L \cdot I_m \cdot \sin[(-\omega) \cdot t + \phi] \cdot \omega + i \cdot I_m \cdot \omega \cdot L \cdot \cos[(-\omega) \cdot t + \phi]$$


or ...


$$I_m = \frac{U_m}{\sqrt{R^2 + (L \cdot \omega)^2}}$$

and ...

$$\phi = \text{atan}\left(\frac{L \cdot \omega}{R}\right)$$

using these relationships in the plot ...

 plotting set up

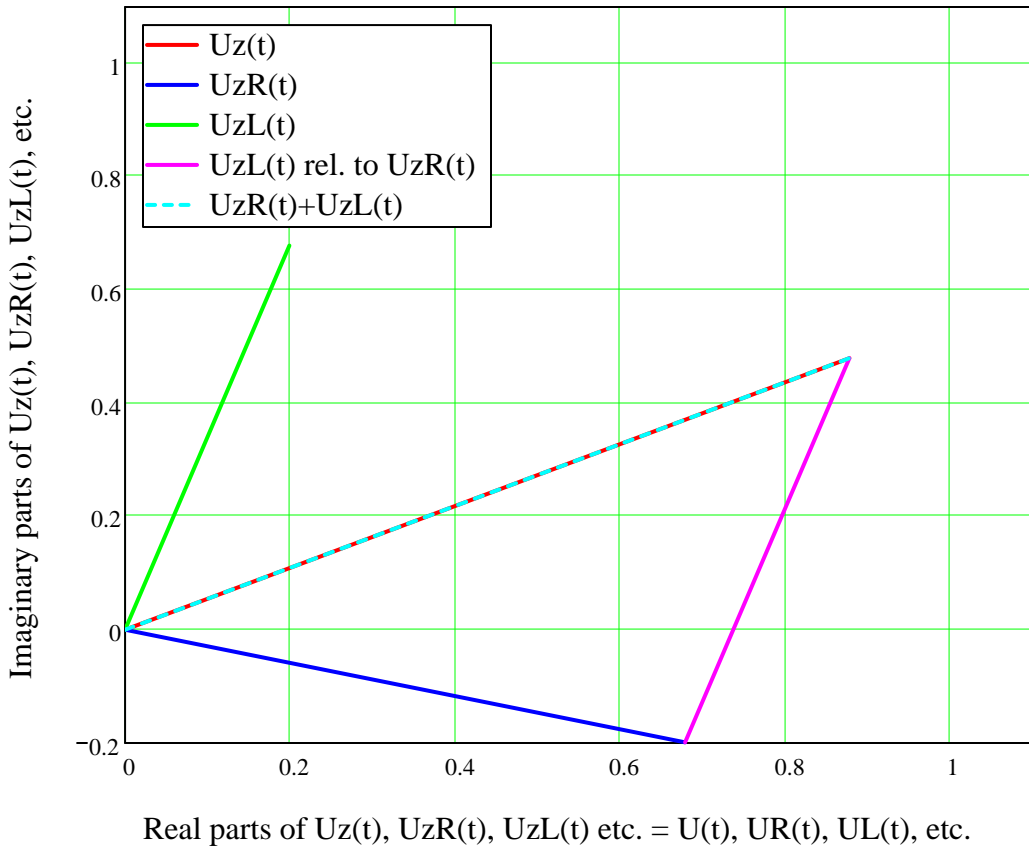

N.B. angle may not appear as right angle due to scales
 ϕ shown as lag (positive value with negative sign)

capacitor lead approach (text)

similar for Capacitance

imposed ... external $U(t) := U_m \cdot \cos(\omega \cdot t)$ $U_m = \text{amplitude_of_voltage}$ $V = 1 \text{ V}$ (2.62)

$\omega = \text{frequency}$ $\text{Hz} = 1 \frac{1}{\text{s}}$ $\text{min} = 60 \text{ s}$

$t = \text{time}$

this is different from text: lag phase angle vs. lead angle used

resulting current assumed also harmonic $I(t) := I_m \cdot \cos(\omega \cdot t - \phi)$ $I_m = \text{amplitude_of_current}$ $V = 1 \text{ V}$


current assumed to have **lag** angle. this approach taken to allow common treatment of L and C in circuits $\phi = \text{phase_lag_angle}$

complex (vector) representation, set up with real part expressed as cos

$U_z(t) = U_m \cdot \cos(\omega \cdot t) + U_m \cdot \sin(\omega \cdot t) \cdot i$ $I_z(t) = I_m \cdot \cos(\omega \cdot t - \phi) + I_m \cdot \sin(\omega \cdot t - \phi) \cdot i$

plotting set up

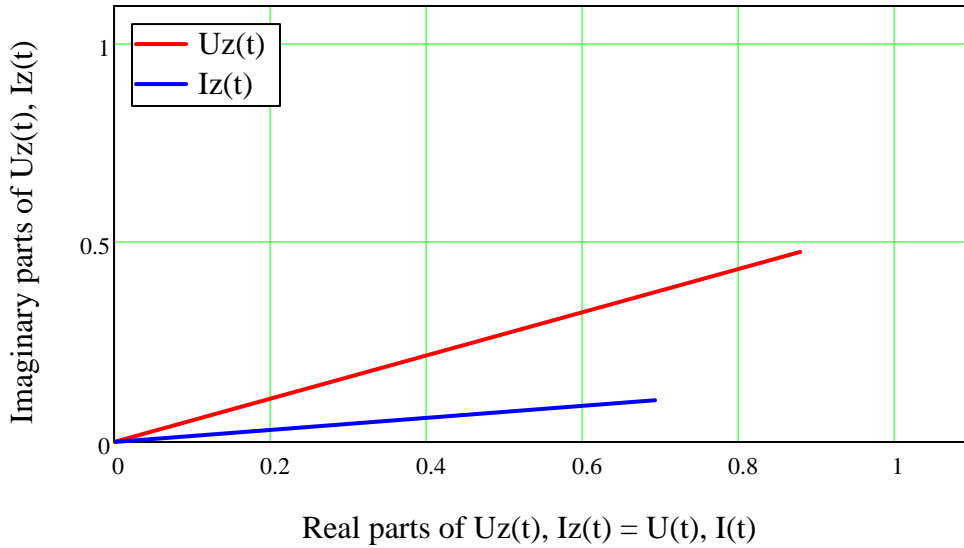voltage and current at $\omega \cdot t$ positive lag phase angle



voltage across capacitor (from above)

$$(2.57) \quad U_C(t) = \int_0^t \frac{I(t)}{C} dt = \int_0^t \frac{I_m \cdot \cos(\omega \cdot t - \phi)}{C} dt = \frac{I_m \cdot \sin(\omega \cdot t - \phi)}{C \cdot \omega} = \frac{I_m}{C \cdot \omega} \cdot \cos\left(\omega \cdot t - \phi - \frac{\pi}{2}\right)$$

using complex (vector) notation


$$U_z(t) := \mathbf{U}_m \cdot \cos(\omega \cdot t) + U_m \cdot \sin(\omega \cdot t) \cdot i \qquad I_z(t) := \mathbf{I}_m \cdot \cos(\omega \cdot t - \phi) + I_m \cdot \cos(\omega \cdot t - \phi) \cdot i$$

$$U_{zC}(t) := \frac{\mathbf{I}_m}{C \cdot \omega} \cdot \cos\left(\omega \cdot t - \phi - \frac{\pi}{2}\right) + \frac{I_m}{C \cdot \omega} \cdot \sin\left(\omega \cdot t - \phi - \frac{\pi}{2}\right) \cdot i$$


$$U_{zR}(t) := R \cdot \mathbf{I}_m \cdot \cos(\omega \cdot t - \phi) + R \cdot I_m \cdot \sin(\omega \cdot t - \phi) \cdot i$$

Kirchoff's second law for resistor with capacitor...

$$U_z(t) := U_{zR}(t) + U_{zC}(t) \rightarrow \Omega \cdot \mathbf{I}_m \cdot \cos[(-\omega) \cdot t + \phi] - i \cdot \Omega \cdot \mathbf{I}_m \cdot \sin[(-\omega) \cdot t + \phi] - \frac{\mathbf{I}_m}{C \cdot \omega} \cdot \sin[(-\omega) \cdot t + \phi] - i \cdot \frac{I_m}{C \cdot \omega} \cdot \cos[(-\omega) \cdot t + \phi]$$

 plotting set up


Voltages with phase angle = - 40 deg

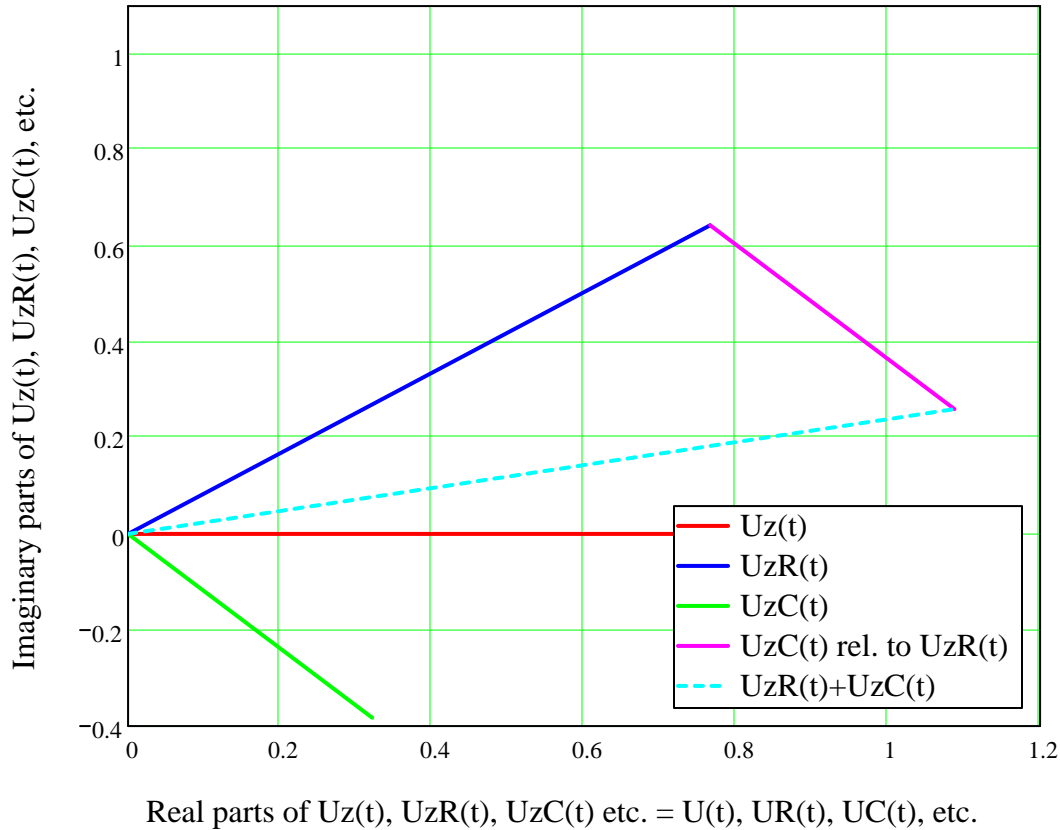


N.B. angle is distorted due to scales; angle between $U_{zR}(t)$ and $U_{zC}(t)$ is $\pi/2$

$$U_z(t) = U_m \cdot \cos(\omega \cdot t) + U_m \cdot \sin(\omega \cdot t) = R \cdot I_m \cdot \cos(\omega \cdot t - \phi) + i \cdot R \cdot I_m \cdot \sin(\omega \cdot t - \phi) + \frac{I_m}{C \cdot \omega} \cdot \sin(\omega \cdot t - \phi) - i \cdot \frac{I_m}{C \cdot \omega} \cdot \cos(\omega \cdot t - \phi)$$

look at solution plotted

 plotting set up

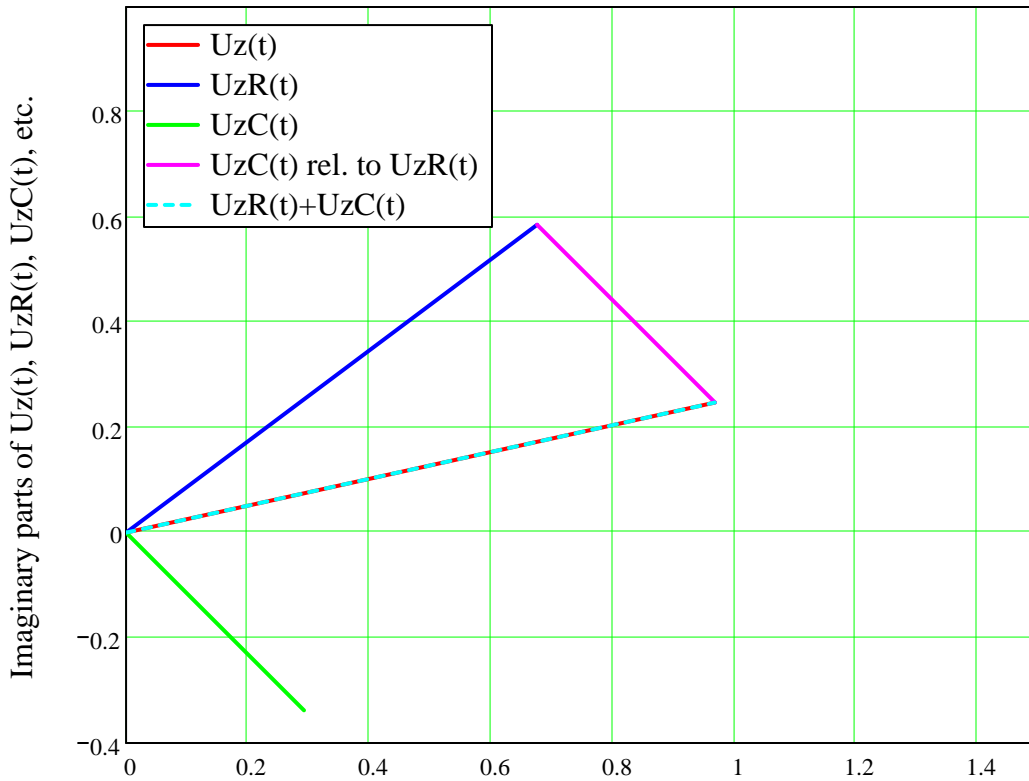

Real parts of $U_z(t)$, $U_{zR}(t)$, $U_{zC}(t)$ etc. = $U(t)$, $U_R(t)$, $U_C(t)$, etc.

$$U_z(t) = U_m \cdot \cos(\omega \cdot t) + U_m \cdot \sin(\omega \cdot t) = R \cdot I_m \cdot \cos(\omega \cdot t - \phi) + i \cdot R \cdot I_m \cdot \sin(\omega \cdot t - \phi) + \frac{I_m}{C \cdot \omega} \cdot \sin(\omega \cdot t + \phi) - i \cdot \frac{I_m}{C \cdot \omega} \cdot \cos(\omega \cdot t + \phi)$$

magnitude similar to above ...

$$I_m = \frac{U_m}{\sqrt{R^2 + \frac{1}{(\omega \cdot C)^2}}}$$

phase angle is negative; hence referred to as **lead** angle

$$\phi = -\text{atan}\left(\frac{1}{\omega \cdot C \cdot R}\right)$$

N.B. angle may not appear as right angle due to scales

ϕ shown as **lead** (negative value with negative sign)

$\phi_1 = -26.565 \text{ deg}$ in this numerical example

so with both L and C

$$\phi = \text{atan}\left(\frac{\omega \cdot L}{R} - \frac{1}{\omega \cdot C \cdot R}\right)$$

Section 2.3.4

Direct current (DC)

$$P = U \cdot I = I^2 \cdot R$$

Single phase alternating current (AC)

$$P(t) = U(t) \cdot I(t)$$

typically sinusoidal ...

$$U(t) := U_m \cdot \cos(\omega \cdot t)$$

$$I(t) := I_m \cdot \cos(\omega \cdot t - \phi)$$

lag phase angle used

$$\text{average power ... } P_a := \lim_{T \rightarrow \infty} \left(\frac{1}{T} \cdot \int_0^T U(t) \cdot I(t) dt \right) \rightarrow \frac{1}{2} \cdot U_m \cdot I_m \cdot \cos(\phi)$$

in practice effective values are used

$$U_e := \lim_{T \rightarrow \infty} \sqrt{\frac{1}{T} \cdot \int_0^T (U_m \cdot \cos(\omega \cdot t))^2 dt} \rightarrow \frac{1}{2} \cdot 2^{\frac{1}{2}} \cdot (U_m^2)^{\frac{1}{2}} \quad U_e := \frac{U_m}{\sqrt{2}} \quad U_e = \text{effective_voltage}$$

$$I_e := \lim_{T \rightarrow \infty} \sqrt{\frac{1}{T} \cdot \int_0^T (I_m \cdot \cos(\omega \cdot t - \phi))^2 dt} \rightarrow \frac{1}{2} \cdot 2^{\frac{1}{2}} \cdot (I_m^2)^{\frac{1}{2}} \quad I_e := \frac{I_m}{\sqrt{2}} \quad I_e = \text{effective_current}$$

so average power becomes ...

$$P_a := U_e \cdot I_e \cdot \cos(\phi)$$

$\cos(\phi) = \text{power_factor}$

what is current required in two systems with same effective voltage but larger phase lag?

here forward e subscript dropped and $U == U_e, I == I_e$

some power and current definitions

$$\text{apparent_power} = V \cdot A = U \cdot I$$

I = current

A = 1 amp

$$\text{real_power} = U \cdot I \cdot \cos(\phi)$$

W = 1 W

same for current

$$\text{load_current} = I \cdot \cos(\phi)$$

A = 1 amp

$$\text{reactive_power} = U \cdot I \cdot \sin(\phi)$$

V·A

$$\text{reactive_current} = I \cdot \sin(\phi)$$

A = 1 amp

three phase alternating current

$$\alpha := \begin{pmatrix} 0 \\ 2 \cdot \frac{\pi}{3} \\ 4 \cdot \frac{\pi}{3} \end{pmatrix}$$

phase angle for respective phases

and ...

ORIGIN := 1

i := 1..3

$$U_{p_i} := U_m \cdot \cos(\omega \cdot t - \alpha_i)$$

$$I_{p_i} := I_m \cdot \cos(\omega \cdot t - \alpha_i - \phi)$$

$$\sum_{i=1}^3 U_{p_i} \text{ expand} \rightarrow 0$$

$$\sum_{i=1}^3 I_{p_i} \text{ expand} \rightarrow 0$$

star connection ...

$$I_{L_1} = I_{p_1}$$

$$I_{L_2} = I_{p_2}$$

$$I_{L_3} = I_{p_3}$$

i := 1..2

$$U_{L_i} := U_{p_i} - U_{p_{i+1}}$$

$$U_{L_3} := U_{p_3} - U_{p_{31}}$$

i := 1..3

$$U_{z_{p_i}} := U_m \cdot \cos(\omega \cdot t - \alpha_i) + U_m \cdot \sin(\omega \cdot t - \alpha_i) \cdot i$$

i := 1..2

$$U_{z_{L_1}} := U_{z_{p_1}} - U_{z_{p_{i+1}}}$$

$$U_{z_{L_3}} := U_{z_{p_3}} - U_{z_{p_1}}$$

i := 1..3 e.g. $U_{z_{L_1}}$ simplify $\rightarrow U_m \cdot \cos(\omega \cdot t) + i \cdot U_m \cdot \sin(\omega \cdot t) + U_m \cdot \cos\left(\omega \cdot t + \frac{1}{3} \cdot \pi\right) + i \cdot U_m \cdot \sin\left(\omega \cdot t + \frac{1}{3} \cdot \pi\right)$
 magnitude is ... from trigonometry...

$$U_m \cdot \sqrt{\left(\cos(\omega \cdot t) + \cos\left(\omega \cdot t + \frac{\pi}{3}\right)\right)^2 + \left(\sin(\omega \cdot t) + \sin\left(\omega \cdot t + \frac{\pi}{3}\right)\right)^2} \text{ expand } \rightarrow \left(3 \cdot \cos(\omega \cdot t)^2 + 3 \cdot \sin(\omega \cdot t)^2\right)^{\frac{1}{2}}$$

magnitude := $U_m \cdot \sqrt{3}$ (2.85)

angle relative to $\omega \cdot t$ (set $\omega \cdot t = 0$)

$$U_{z_{L_1}} \left| \begin{array}{l} \text{simplify} \\ \text{substitute, } t = 0 \end{array} \right. \rightarrow U_m \cdot \cos(0) + i \cdot U_m \cdot \sin(0) + U_m \cdot \cos\left(\frac{1}{3} \cdot \pi\right) + i \cdot U_m \cdot \sin\left(\frac{1}{3} \cdot \pi\right)$$


$$\text{angle}_{\omega t} = \text{atan}\left(\frac{\sin\left(\frac{\pi}{3}\right)}{1 + \cos\left(\frac{\pi}{3}\right)}\right)$$

$$\text{atan}\left(\frac{\sin\left(\frac{\pi}{3}\right)}{1 + \cos\left(\frac{\pi}{3}\right)}\right) = 30 \text{ deg}$$

for plotting ... i := 1..3 $\omega_1 := 1$ $t_1 := 0.79$

$$\phi_1 := 1 \quad U_{1_{p_i}} := 1 \quad U_{1_{p_i}} := U_{1_m} \cdot \cos(\omega_1 \cdot t_1 - \alpha_i)$$
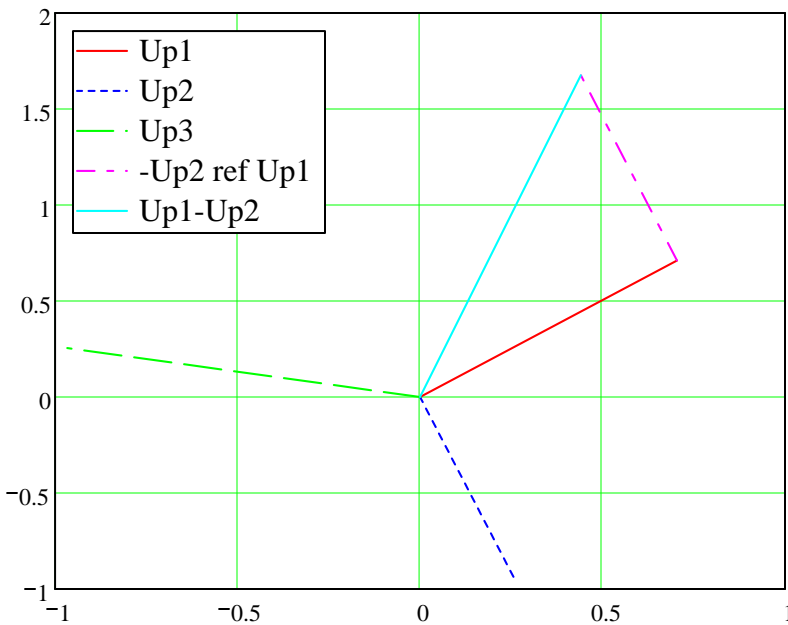
$$U_{1z_{p_i}} := U_{1_m} \cdot \cos(\omega_1 \cdot t_1 - \alpha_i) + U_{1_m} \cdot \sin(\omega_1 \cdot t_1 - \alpha_i) \cdot i$$



similarly in a delta connection ... current has same geometry

$$U_L = U_p \quad (2.86)$$

$$I_L = I_p \cdot \sqrt{3} \quad (2.87)$$

2.3.5 Magnetic induction


$$B = \mu \cdot \frac{I}{2 \cdot \pi \cdot r} \quad B = \text{flux_density} \quad T = 1 \text{ tesla} \quad T = 1 \frac{\text{Wb}}{\text{m}^2} \quad T = 1 \frac{\text{kg}}{\text{amp} \cdot \text{s}^2}$$

(2.90)

$$\mu = \text{permeability_of_medium} \quad \frac{\text{H}}{\text{m}} = 1 \frac{\text{m} \cdot \text{kg}}{\text{A}^2 \cdot \text{s}^2} \quad \frac{\text{H}}{\text{m}} = 1 \frac{\text{henry}}{\text{m}}$$

$$\mu = \mu_0 \cdot \mu_R \quad \mu_0 = \text{permeability_of_vacuum} \quad \mu_0 := 4 \cdot \pi \cdot 10^{-7} \frac{\text{H}}{\text{m}}$$

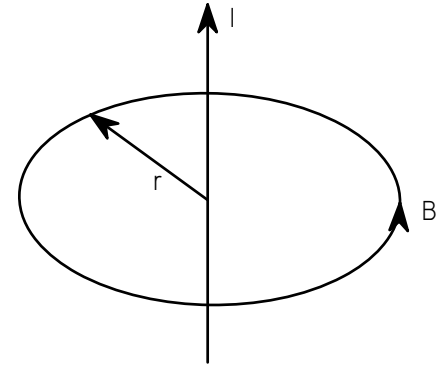$\mu_R = \text{permeability_of_medium_relative_to_vacuum}$ unitless
 derived from Biot-Savart law



magnetic field around wire carrying current

e.g. magnetic field at point P results from motion of charged particle at velocity V in vacuum

	<u>parameters</u>	<u>units and equivalents</u>
$B = \frac{\mu_0}{4 \cdot \pi} \cdot q \cdot \frac{\vec{V} \times \vec{a}_r}{r^2} \quad T$	$B = \text{flux_density}$ $\mu_0 = \text{permeability_in_vacuum}$ $q = \text{charge}$ $\vec{V} = \text{velocity_vector_of_charge}$ $\vec{a}_r = \text{unit_vector_from_charge_q_to_point_P}$ $r = \text{distance_from_P_to_charge}$	$T = 1 \text{ tesla} \quad T = 1 \times 10^4 \text{ gauss} \quad T = 1 \frac{1}{\text{m}^2} \text{ Wb}$ $\mu_0 := 4 \cdot \pi \cdot 10^{-7} \frac{\text{H}}{\text{m}} \quad \frac{\text{H}}{\text{m}} = 1 \frac{\text{N}}{\text{A}^2} \quad \frac{\text{H}}{\text{m}} = 1 \frac{\text{newton}}{\text{amp}^2}$ $C = 1 \text{ coul} \quad C = 1 \text{ A} \cdot \text{s}$ $\frac{\text{m}}{\text{s}}$ <p style="text-align: right;">units check</p> $\frac{\text{H}}{\text{m}} \cdot \text{C} \cdot \frac{\text{m}}{\text{s}} \cdot \frac{1}{\text{m}^2} = 1 \text{ T}$

differential form

$$dB = \frac{\mu_0}{4 \cdot \pi} \cdot dq \cdot \frac{\vec{V} \times \vec{a}_r}{r^2}$$

line currents ...

$$q \cdot \vec{V} = I \cdot d\vec{l}$$

so ..

$$dB = \frac{\mu_0}{4 \cdot \pi} \cdot I \cdot \frac{d\vec{l} \times \vec{a}_r}{r^2} \quad B = \int \frac{\mu_0}{4 \cdot \pi} \cdot \frac{I}{r^2} d\vec{l} \times \vec{a}_r$$

e.g. long straight wire with current I

$$dB = \frac{\mu_0}{4 \cdot \pi} \cdot I \cdot \frac{\vec{dl} \times \vec{a}_r}{r^2} = \frac{\mu_0}{4 \cdot \pi} \cdot I \cdot \frac{dl \cdot \sin(\theta)}{r^2}$$

see figure at right

$$dl \cdot \sin(\theta) = r \cdot d\alpha$$

$$\frac{dl \cdot \sin(\theta)}{r^2} = \frac{r \cdot \frac{d\alpha}{\sin(\theta)} \cdot \sin(\theta)}{r^2} = \frac{d\alpha}{r}$$

$$r = \frac{R}{\cos(\alpha)} \quad \frac{d\alpha}{r} = \frac{\cos(\alpha) \cdot d\alpha}{R}$$

$$dB = \frac{\mu_0}{4 \cdot \pi} \cdot I \cdot \frac{\vec{dl} \times \vec{a}_r}{r^2} = \frac{\mu_0}{4 \cdot \pi} \cdot I \cdot \frac{dl \cdot \sin(\theta)}{r^2} = \frac{\mu_0}{4 \cdot \pi} \cdot I \cdot \frac{\cos(\alpha) \cdot d\alpha}{R}$$

$$B = \int 1 dB = \int_{-\frac{\pi}{2}}^{\frac{\pi}{2}} \frac{\mu_0}{4 \cdot \pi} \cdot I \cdot \frac{\cos(\alpha)}{R} d\alpha$$


$$\int_{-\frac{\pi}{2}}^{\frac{\pi}{2}} \frac{\mu_0}{4 \cdot \pi} \cdot I \cdot \frac{\cos(\alpha)}{R} d\alpha \rightarrow \frac{1}{2} \cdot \frac{\mu_0}{\pi} \cdot \frac{I}{R}$$

$$B = \frac{\mu_0 \cdot I}{2 \cdot \pi \cdot R} \quad \text{Q.E.D.}$$

if area not vacuum, substitute $\mu = \mu_r \cdot \mu_0 \dots$

magnetic flux density over an area AA
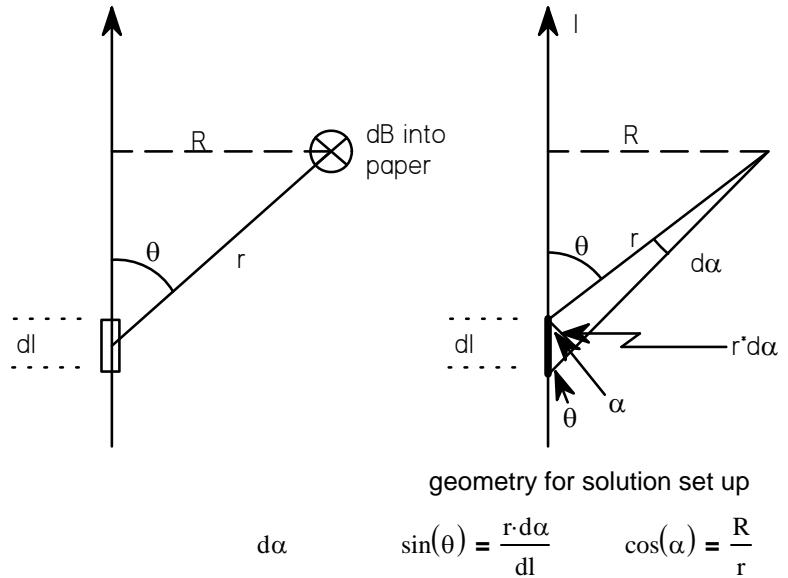
$$\Phi := \int \mathbf{B} \cdot d\mathbf{AA} \quad \mathbf{AA} = \text{enclosed_area} \quad \text{to distinguish from A (ampere)} \quad \text{Wb} = 1 \text{ weber} \quad \text{Wb} = 1 \frac{\text{kg} \cdot \text{m}^2}{\text{A} \cdot \text{s}^2} \quad \text{A} = 1 \text{ amp}$$



Lorentz force


a force will act on a current carrying conductor when it is placed in a magnetic field

$$F_L = B \cdot I \cdot \text{len} \quad F_L = \text{Lorentz_force} \quad N = 1 \text{ newton}$$



$$(2.92) \quad B = \text{flux_density} \quad T = 1 \text{ tesla}$$

$$I = \text{current_thru_conductor} \quad A = 1 \text{ amp}$$

$$\text{len} = \text{length} \quad m$$

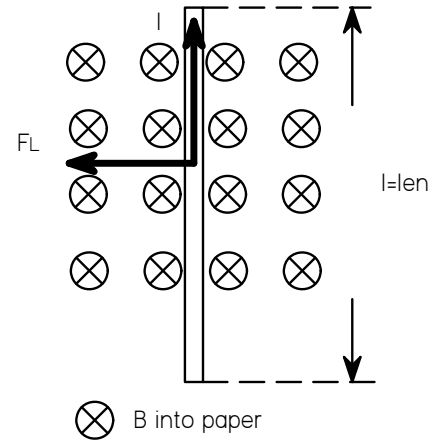

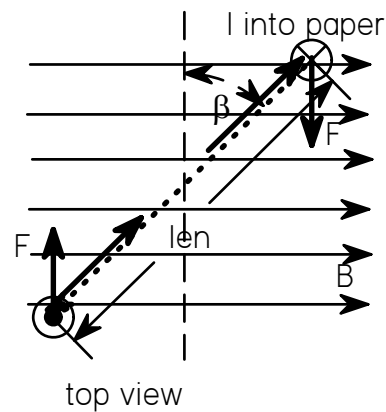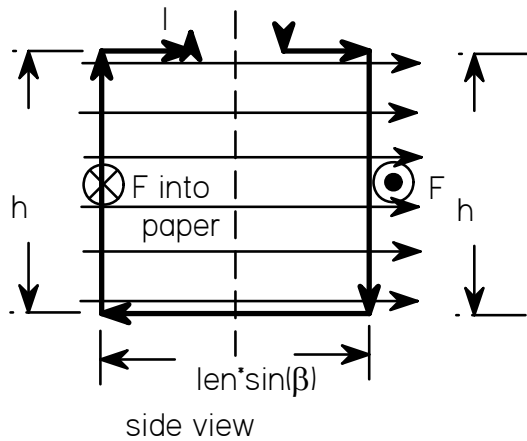$F_L = I \cdot \text{len} \times B$ where \times is vector cross product and magnitude is $B \cdot I \cdot \sin(\text{angle})$ right hand rule applies
view of single coil in magnetic field (B) with current (I) (slightly revised from text; $\text{len} \cdot \sin(\beta)$)



force on one segment (h) of coil

$$F = I \times B \cdot h$$

N.B. I is perpendicular to B => $F = I \cdot B \cdot h$

torque on coil depends on β

$$M = F \cdot \text{len} \cdot \sin(\beta)$$

$\text{len} \cdot \sin(\beta) = \text{distance_between_couple_of_force_F}$

$$M = F \cdot \text{len} \cdot \sin(\beta) = I \cdot B \cdot h \cdot \text{len} \cdot \sin(\beta) = I \cdot B \cdot \text{AA} \cdot \sin(\beta) = I \cdot \Phi \cdot \sin(\beta)$$

AA = area_of_coil = enclosed_area AA to distinguish from A (ampere)

account for multiple windings (turns) (N)

$$M = N \cdot I \cdot \Phi \cdot \sin(\beta)$$

general relationship recognizing proportionality to $I \cdot \Phi$

$$M = K_m \cdot \Phi \cdot I \quad K_m = \text{constant_for_given_motor} \quad (2.93)$$

Faraday's Law

Voltage is generated in conductor when moving in magnetic field

$$E = -B \cdot \text{len} \cdot v$$

E = induction_potential = electromotive_force V = 1 volt


B = flux_density T = 1 tesla

v = velocity $\frac{m}{s}$

len = length_of_conductor m

units check
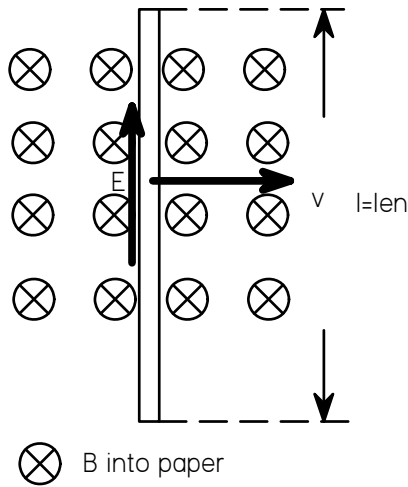
$$T \cdot \frac{m}{s} \cdot m = 1 \text{ V}$$



E as shown is positive value and direction minus sign is consistent with observation that E as shown would produce a current in the same direction which in turn would produce a force opposite to velocity.

vector form ... $E = -(B \times v) \cdot \text{len}$

consistent with text ... multiply by $\sin(\alpha)$ where α is angle between B and v

may also be expressed as ... $E = \frac{d}{dt} \Phi$ for single turn and .. $E = -N \frac{d}{dt} \Phi$ $\frac{Wb}{s} = 1 \text{ V}$ (2.95)

since ... $\Phi = B \cdot \text{Area}$ $E = \frac{d}{dt} \Phi = \frac{d}{dt} (B \cdot \text{Area}) = -B \frac{d}{dt} \text{Area} = -B \cdot \text{len} \frac{d}{dt} x$ as ... $\text{Area} = \text{len} \cdot x$

in coil rotating in constant magnetic field B $\Phi = B \cdot \text{Area} \cdot \cos(\beta) = B \cdot \text{Area} \cdot \cos(\omega \cdot t)$ where ...
 Area = area_enclosed_in_coil

and with N turns ... $E = -N \frac{d}{dt} (B \cdot \text{Area} \cdot \cos(\omega \cdot t)) \rightarrow E = N \cdot B \cdot \text{Area} \cdot \sin(\omega \cdot t) \cdot \omega$

substituting ... $\omega = 2 \cdot \pi \cdot n$ n = rpm rpm = 6.283 $\frac{\text{rad}}{\text{min}}$ $E = N \cdot 2 \cdot \pi \cdot n \cdot B \cdot \text{Area} \cdot \sin(\omega \cdot t)$

as above for motor constant ... express ... $E = K_E \cdot \Phi \cdot n$ $K_E = \text{constant_for_given_motor}$

E = induced_electromotive_force V = 1 volt

Φ = magnetic_flux Wb = 1 weber

n = rotation_speed rpm = 0.105 $\frac{1}{\text{sec}}$ 1 Wb · 60rpm = 6.283 V