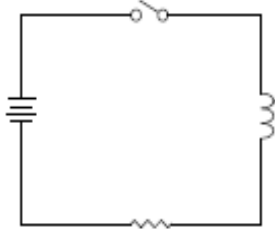


8.022 Lecture Notes Class 36 - 11/21/2006



RLC (Undriven)

V across capacitor

$$I = -\frac{dq}{dt}$$

$$Q = CV$$

$$V = L\frac{dI}{dt} + IR$$

$$I = -C\frac{dV}{dt} \quad \left(\frac{d}{dt}(Q = CV)\right)$$

$$V = L\frac{d^2V}{dt^2}C + RC\frac{dV}{dt}$$

$$\frac{d^2V}{dt^2} + \frac{R}{L}\frac{dV}{dt} + \frac{1}{LC}V = 0$$

Try

$$V = Ae^{-\alpha t} \cos \omega t$$

$$\begin{aligned}\frac{dV}{dt} &= Ae^{-\alpha t}(-\alpha \cos \omega t - \omega \sin \omega t) \\ \frac{d^2V}{dt^2} &= Ae^{-\alpha t}[(\alpha^2 - \omega^2) \cos \omega t + 2\alpha\omega \sin \omega t]\end{aligned}$$

$$(\alpha^2 - \omega^2) \cos \omega t + 2\alpha\omega \sin \omega t - \frac{R}{L}(\alpha \cos \omega t + \omega \sin \omega t) + \frac{1}{LC} \cos \omega t = 0$$


$$\begin{cases} 2\alpha\omega - \frac{R\omega}{L} = 0 \Rightarrow \alpha = \frac{R}{2L} \longrightarrow R \\ \alpha^2 - \omega^2 - \frac{\alpha R}{L} + \frac{1}{LC} = 0 \end{cases}$$

$$\omega^2 = \frac{R^2}{4L^2} - \frac{R^2}{2L^2} + \frac{1}{LC} = \frac{1}{LC} - \frac{R^2}{4L^2}$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

$$R < 2\sqrt{4c}$$
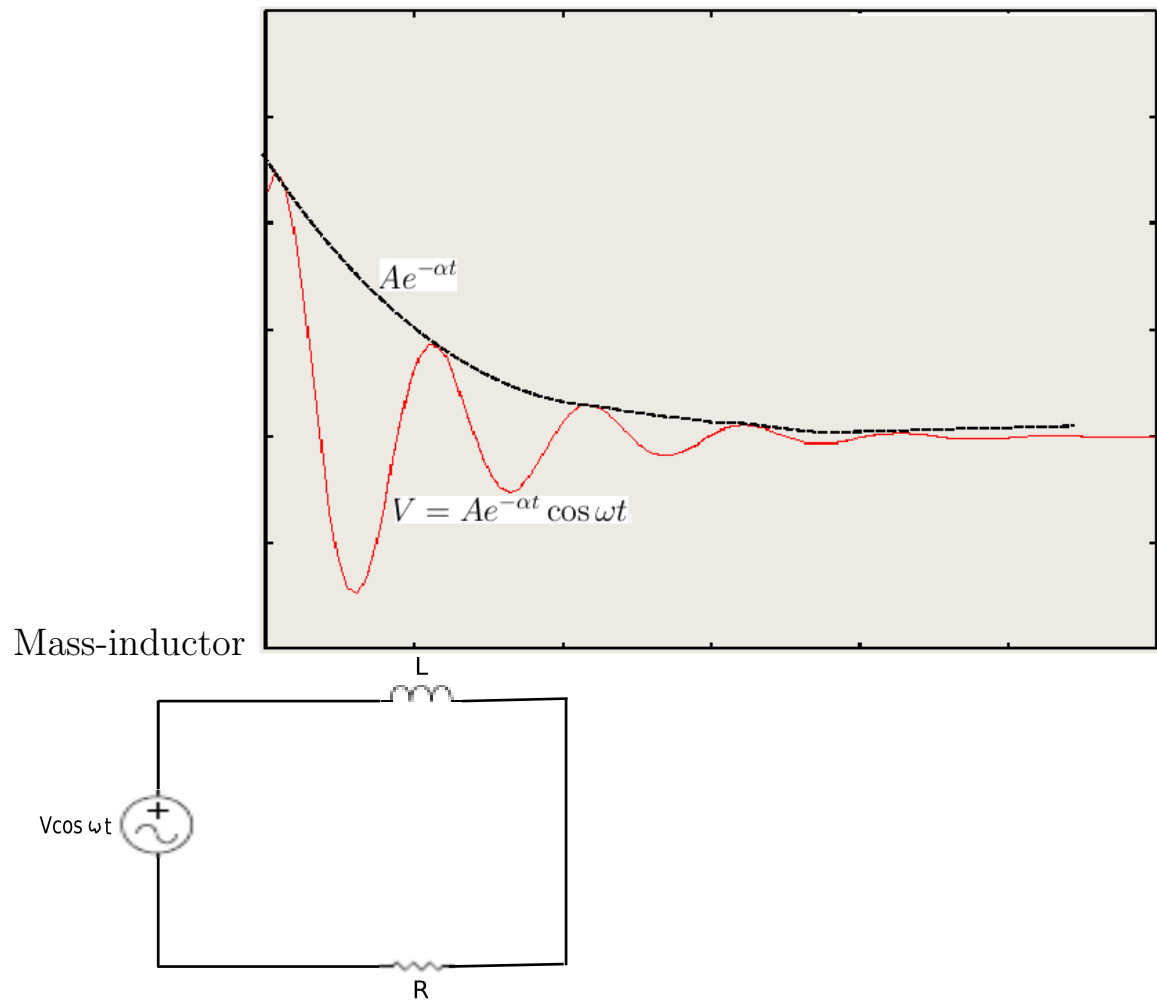
$$\longrightarrow \omega = \sqrt{\frac{1}{LC}}$$



$$V \cos \omega t = L \frac{dI}{dt} + RI$$

$$I = I \cos(\omega t + \phi)$$